 


Gates and Boolean Algebra


Read: Appendix C (4th edition) or Appendix B (5th edition), sections 1, 2, and 3 (partial) — pages 1 to 13.

- NOT — unary operator, written as a bar over the variable.
 - Example: \overline{a} , true (1) if a is 0.
 - NOT gate ($c = \overline{a}$).
 - There are two different drawings used for NOT.

a	$c = \overline{a}$
0	1
1	0




 - AND — written as \bullet
 - Example: $A \bullet B$, true (1) only if both A and B are 1.
 - AND gate ($c = a \text{ AND } b, c = a \bullet b$).




a	b	$c = a \bullet b$
0	0	0
0	1	0
1	0	0
1	1	1

 - OR — written as $+$
 - Example: $A + B$, true (1) if at least one of A or B is 1.
 - OR gate ($c = a \text{ OR } b, c = a + b$)




a	b	$c = a + b$
0	0	0
0	1	1
1	0	1
1	1	1

- Some examples:

 


- NAND — not and:

 


a	b	$c = a \text{ NAND } b$
0	0	1
0	1	1
1	0	1
1	1	0

- NOR — not or:

 


a	b	$c = a \text{ NOR } b$
0	0	1
0	1	0
1	0	0
1	1	0

- XOR — exclusive or:

 

a	b	c = a XOR b
0	0	0
0	1	1
1	0	1
1	1	0

 - It is possible to implement all the other types of gates from NAND gates, or from NOR gates.
 - Simplifies the underlying structure
 - For example, an AND gate can be constructed from two NAND gates:



Binary Addition


Read: Appendix C (4th edition) or Appendix B (5th edition), section 5 — pages 26 to 35.

Binary Addition, first attempt:

- Need to compute $a + b$ to get the sum, and the carry:


A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 - Here is one solution using one XOR and one AND gate:




Binary Addition, first attempt (continued):

 - Here is a second solution. This one starts by computing the Sum bit. It uses two AND gates, one OR gate, and two NOT gates (do you see the NOT gates?):




- Then, to get the Carry bit:

 


A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Binary Addition, first attempt (continued):

 - Put the two parts from the previous slide together:



 
- Either of these two solutions is a *Half Adder*.
 - It adds the two binary digits producing the correct sum and carry results.
 - To simplify drawing the picture, we use:



Binary Addition, first attempt (continued):


1101
+0011

Inputs			Outputs	
A	B	Carry In	Carry Out	Sum
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1

 


Binary Addition, first attempt (continued):

 
- Again, we use a simplified drawing to represent the *full adder*:



 - We can hook Full Adder's together to add more than one pair of bits:


 
$$\begin{array}{r}
 1 \\
 a = 1010 \\
 + b = 1101 \\
 \hline
 s = 0111, \text{ carry out} = 1
 \end{array}$$



Binary Addition, first attempt (continued):


- This is called a Ripple Adder.
 - Note how the Carry has to “ripple” through for each bit.
 - Implies that each bit cannot compute its sum until all the previous bits have finished.
 - This can be extended to any number of bits: 8, 16, 32, 64, ...
 - Ripple adders are vvveerrryyy ssslllooowww.
 - We will see a much better solution later.

```
      1001 0110 0110 0111
+   1011 1001 1001 1100
      1001 0110    0110 0111
+  1011 1001 + 1001 1100
```



Multiplexor (Selector).

- The output equals one of the inputs as determined by the *selector* or *control* input.

a	b	s	Output
0	0	0	0
1	0	0	1
0	1	0	0
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

 

  - Construction of a two-input multiplexor:



Summary, thus far:

- There are three key types of logic gate: AND, OR, NOT.
- All three can be implemented in terms of NAND gates, or in terms of NOR gates.
- Logic gates can be assembled to form circuits.
 - We have already covered how to create *half-adders*, *full-adders*, and *multiplexors* using AND, OR, and NOT gates.
- Such circuits can be used to store and manipulate binary information.

Boolean Algebra:

Reading: Section C.2 (4th edition), Section B.2 (5th edition)

- Reminder:
 - OR — written as +
 - Example: $A + B$, true (1) if at least one of A or B is 1.
 - AND — written as •
 - Example: $A \cdot B$, true (1) only if both A and B are 1.
 - NOT — unary operator, written as a bar over the variable.
 - Example: \overline{A} , true (1) if A is 0.
- Useful laws of Boolean Algebra (see page C-6, 4th edition)
 - Identity law: $A + 0 = A$ and $A \cdot 1 = A$.
 - Zero and One laws: $A + 1 = 1$ and $A \cdot 0 = 0$.
 - Inverse laws: $A + \overline{A} = 1$ and $A \cdot \overline{A} = 0$.
 - Commutative laws: $A + B = B + A$ and $A \cdot B = B \cdot A$.
 - Associative laws: $A + (B + C) = (A + B) + C$ and $A \cdot (B \cdot C) = (A \cdot B) \cdot C$.
 - Distributive laws: $A \cdot (B + C) = (A \cdot B) + (A \cdot C)$ and $A + (B \cdot C) = (A + B) \cdot (A + C)$


Boolean Algebra (continued):

- Problem: Construct a logic circuit for a device with three inputs: A, B, and C. The circuit will have three outputs: D, E, and F.
 - Output D as true (1) if at least one input is true. $D = A + B + C$
 - Output E as true (1) if exactly two inputs are true. $E = (\overline{A} \cdot B \cdot C) + (A \cdot \overline{B} \cdot C) + (A \cdot B \cdot \overline{C})$
 - Output F as true (1) if all three inputs are true. $F = A \cdot B \cdot C$
- The truth table for D, E, and F:


A	B	C	D	E	F
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	1	1	0
1	1	1	1	0	1

Boolean Algebra (continued):


- $D = A + B + C$

 

 
In the future, we will represent multi-input OR gates as:



- $F = A \cdot B \cdot C$

 


 In the future, we will represent multi-input AND gates as:



Boolean Algebra (continued):

 - Using the three-input OR and AND gates, we can construct the circuit for E:
 - $E = (\overline{A} \cdot B \cdot C) + (A \cdot \overline{B} \cdot C) + (A \cdot B \cdot \overline{C})$



- How to construct one circuit for computing all three outputs: D, E, F?
 - Combine the three circuits we have already built!
 - The only hard part is drawing the lines for A, B, and C to show where they cross over each other :-).
- Using multi-input AND and OR gates simplifies the drawing of circuits.
 - Importance of abstraction: Once we know how to construct the interior details, we no longer show those details!


Boolean Algebra (continued):

V = Voltage = energy of one electron

i = Current = # of electrons/sec

amp = ampere

Power = iV

 

⊕ Two wires that cross
but do **not** touch.

⊙ Two wires that
are connected.

Constructing an Arithmetic Logic Unit


ALU Overview:

Reading: Section C-5 (4th edition) or Section B-5 (5th edition) — pages 26 to 35.

- The ALU that we will construct will:
 - Take two 32-bit input values, A and B.
 - Output one 32-bit output value C, and a single additional bit Z.
 - Compute the following operations:
 - Bit-wise Logical OR: $C = A \mid B$
 - Bit-wise Logical AND: $C = A \& B$
 - Addition: $C = A + B$
 - Subtraction: $C = A - B$
 - Set Less Than: if $(A < B)$ then $C = 1$ else $C = 0$
 - If Equal: if $(A == B)$ then $Z = 1$ else $Z = 0$


ALU Overview (continued):

- Where the ALU fits into the CPU:
 - The ALU is one part of the CPU.
 - ALU handles arithmetic (add, subtract) and logical (and, or) operations.
 - Inputs to the ALU come from registers.
 - Result of the ALU (generally) goes to a register.
- 15 bits of an instruction specify the registers:
 - 2 source registers (values to read).
 - 1 destination register (value to write).
- ALU operation needs 3 bits to control the ALU.
 - Will be a total of 5 operations.

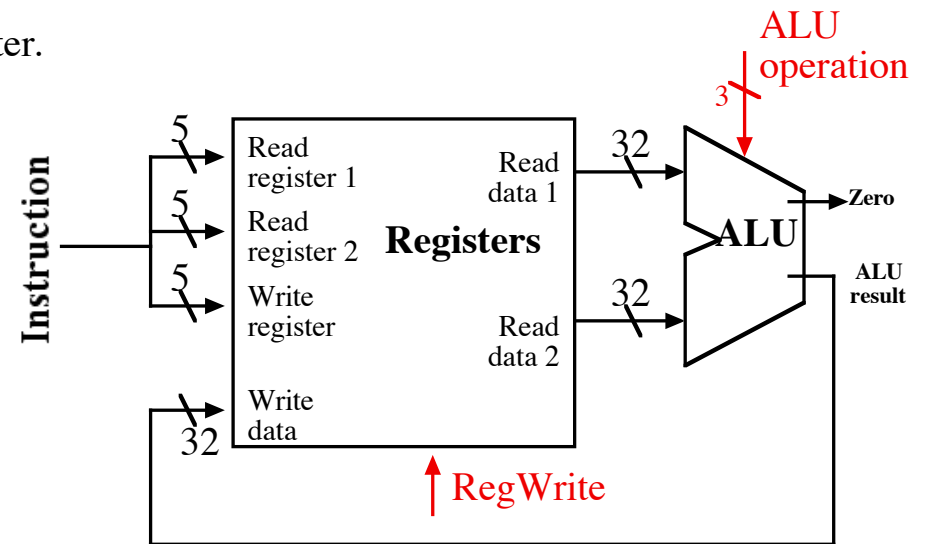

ALU Logical operations:

 
- Need the ability to do AND and OR operation on each pair of bits.
 - One bit from operand A; one bit from operand B.
- Need a multiplexor to choose the desired result.
 - Both operations computed each time.
 - Need to choose only one result.
- To compute a 32-bit result from two 32-bit operands:
 - Replicate the unit shown at right 32 times!



ALU Arithmetic operations:


- From Slide 9:
 - Combined two half-adders, plus one OR gate.
 - Six AND gates, three OR gates, four NOT gates.
 - 13 gates total. 6 gates on the longest path
- There are other ways to approach this problem.

Inputs			Outputs	
A	B	Carry In	Carry Out	Sum
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1

 

ALU Arithmetic operations (continued):

- When is Carry Out true?
 - If two of the inputs are one, or if all three are 1.
- $\text{CarryOut} = (a \cdot b \cdot \overline{\text{CarryIn}}) + (\overline{a} \cdot b \cdot \text{CarryIn}) + (a \cdot \overline{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$
- Could use a 3-input AND gate for each of the four terms.
 - One input to each of the first three AND gates would be negated.
- Instead, we can optimize and use 2-input AND gates, leaving out the negated term each time.
- Why does this work?
 - Leaving out the negate in the 3 AND gates results in true at all 3 AND gates when all 3 inputs are true.

 

Three AND gates.
One 3-input OR gate.

Total: 3 AND + 2 OR gates
= 5 gates


ALU Arithmetic operations (continued):

- When is Sum true (1)?
 - If exactly one of the three inputs (a, b, CarryIn) is true, or if all three are true:

$$\text{Sum} = (\overline{a} \cdot b \cdot \overline{\text{CarryIn}}) + (a \cdot \overline{b} \cdot \overline{\text{CarryIn}}) + (\overline{a} \cdot \overline{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$

- Four AND gates (3 inputs each), one OR gate (4 inputs), three NOT gates:

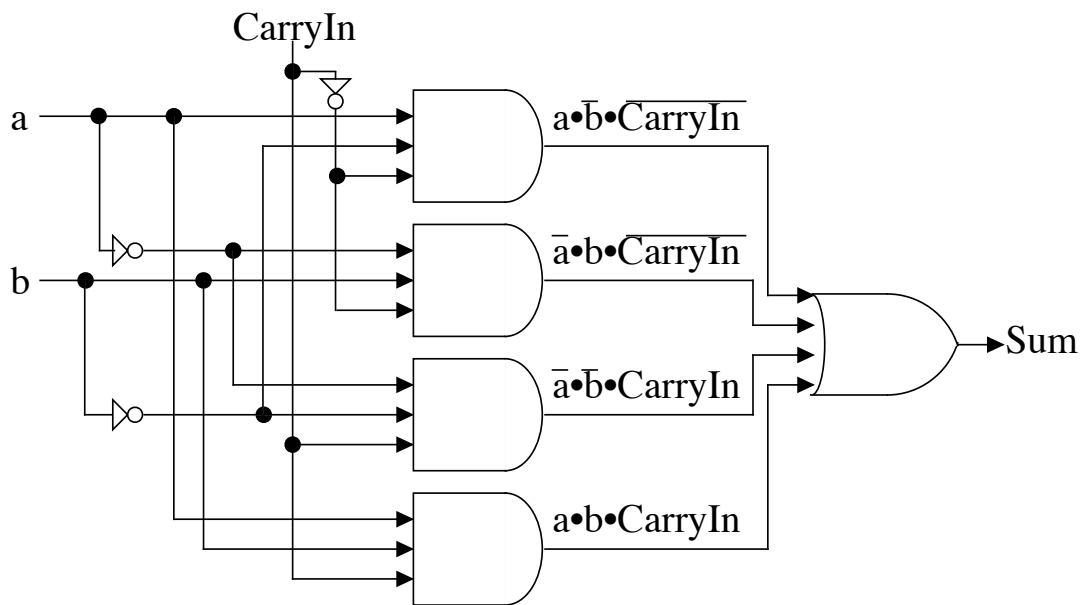
- Total: 4 * 2 AND gates + 3 OR gates + 3 NOT gates = 14 gates



Inputs			Outputs	
A	B	Carry In	Carry Out	Sum
0	0	0	0	0
0	1	0	0	1
1	0	0	0	1
1	1	0	1	0
0	0	1	0	1
0	1	1	1	0
1	0	1	1	0
1	1	1	1	1



ALU Arithmetic operations (continued):

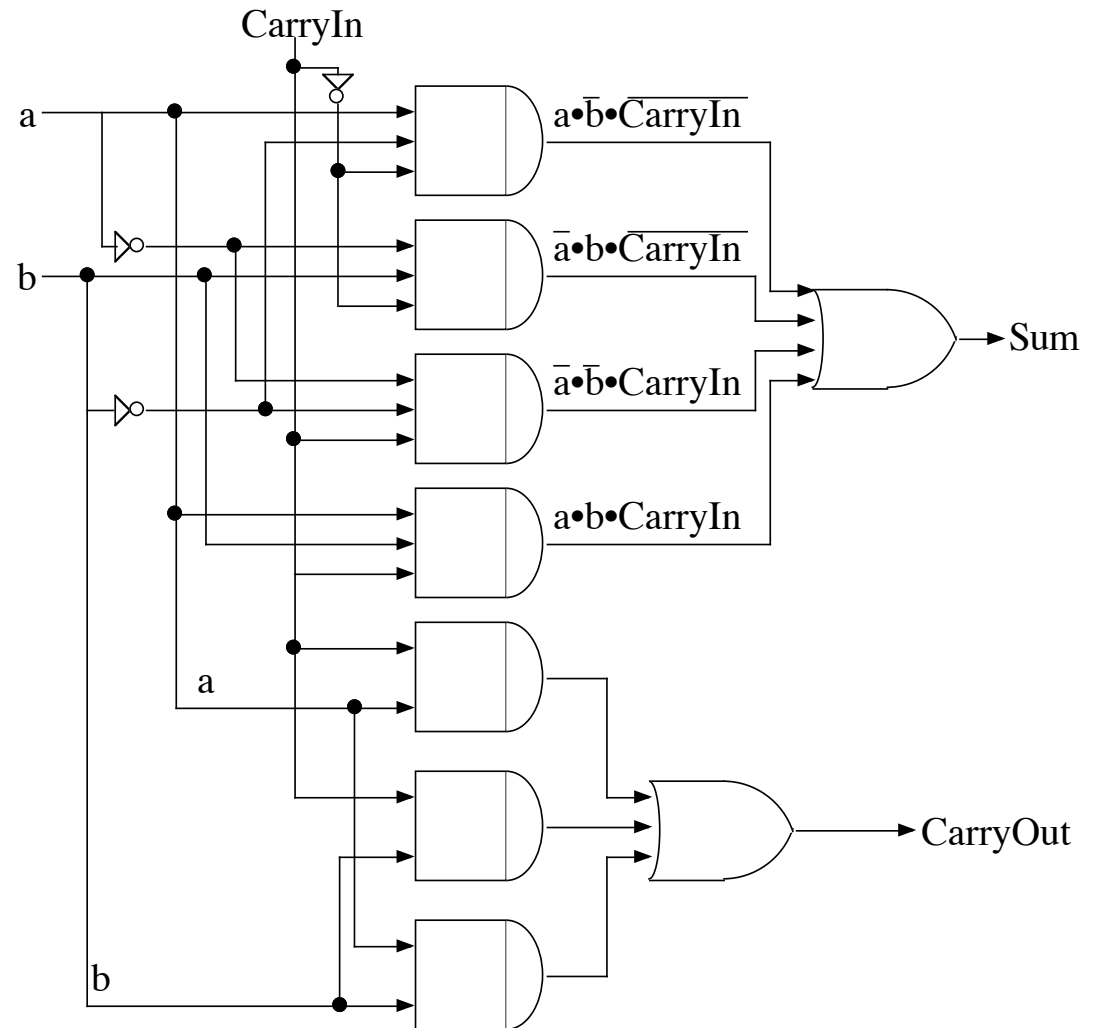- Combined result of Sum and Carry bits.
 - Eleven AND gates.
 - Five OR gates.
 - Three NOT gates.
 - 19 gates total
- Earlier adder version used 13 gates.
- Where is the advantage?
 - We can compute the Sum bit and the CarryOut bit simultaneously.
 - Was done one after the other in the earlier version.




One-bit ALU: supports AND, OR, ADD:

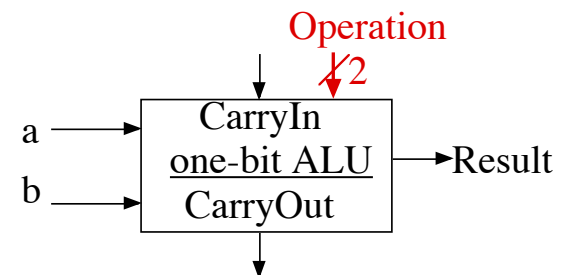 - Outputs:
 - 0: Result of AND.
 - 1: Result of OR.
 - 2: Result of ADD.
 - Includes CarryOut
- Note: All results are computed every time.
 - The Multiplexor allows the unit to send only one result to output.





Combine one-bit ALU's to create 32 bit ALU:

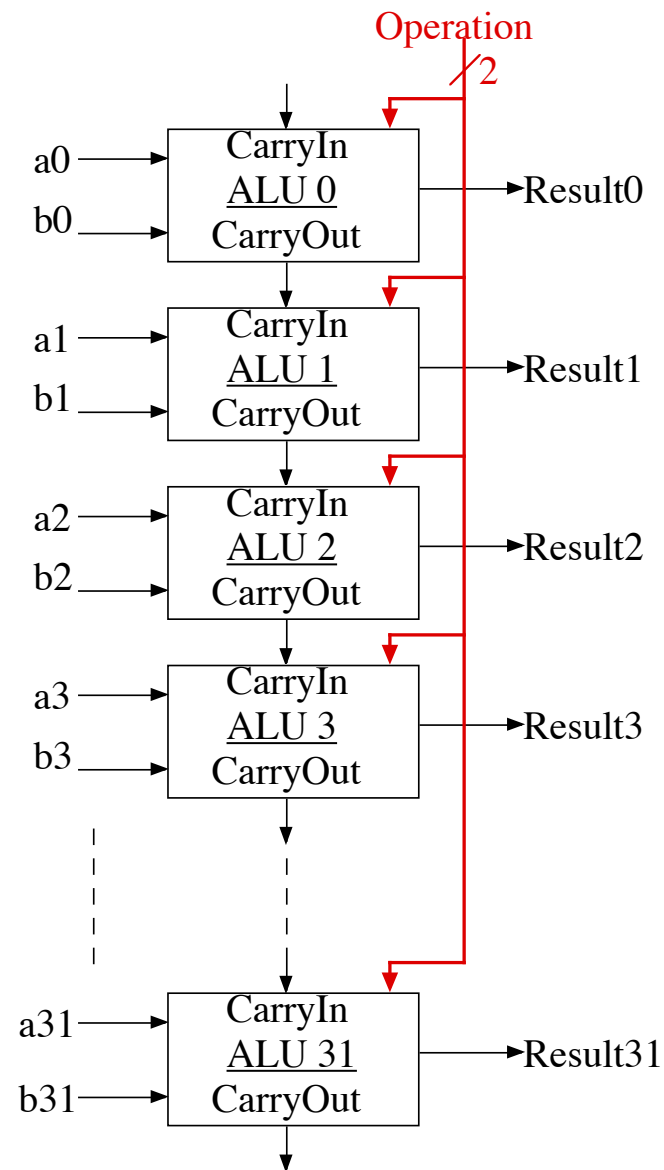- Called a *Ripple Addder*.
- Figure B.5.7, page B-30.
- Drawback: Takes time to “ripple” the carry out bit through all 32 adders.



Subtraction:

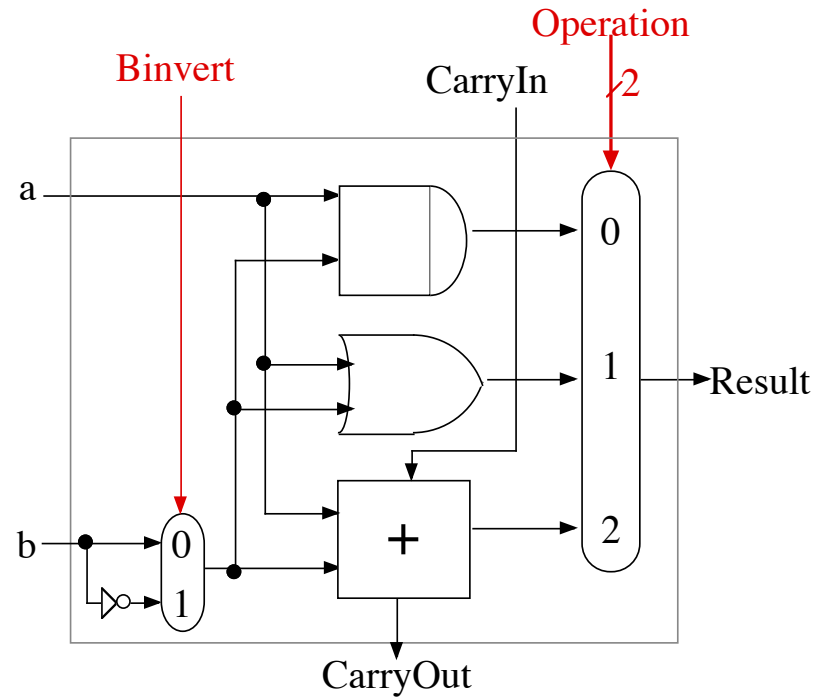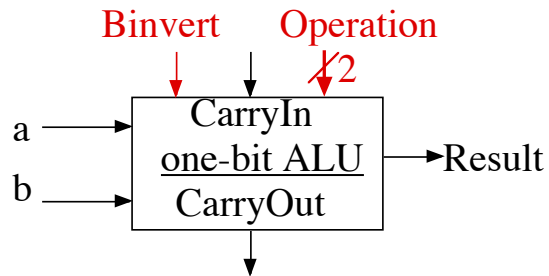
- Two's complement approach: Find the two's complement of b, then add.
 - Two parts:
 - Invert step.
 - Add 1 step.
 - Invert step is easy:



Subtraction (continued):

- Add 1 step (to get two's complement of input b):
 - Put 1 as the CarryIn to ALU 0.
 - Do this by connecting the Binvert control line to CarryIn for ALU 0.
- Since Binvert is now really Bnegate, change its name.
- Thus, to do subtraction:
 - Set Bnegate to 1.
 - Set Operation to ADD.

$$a - b = a + (-b)$$

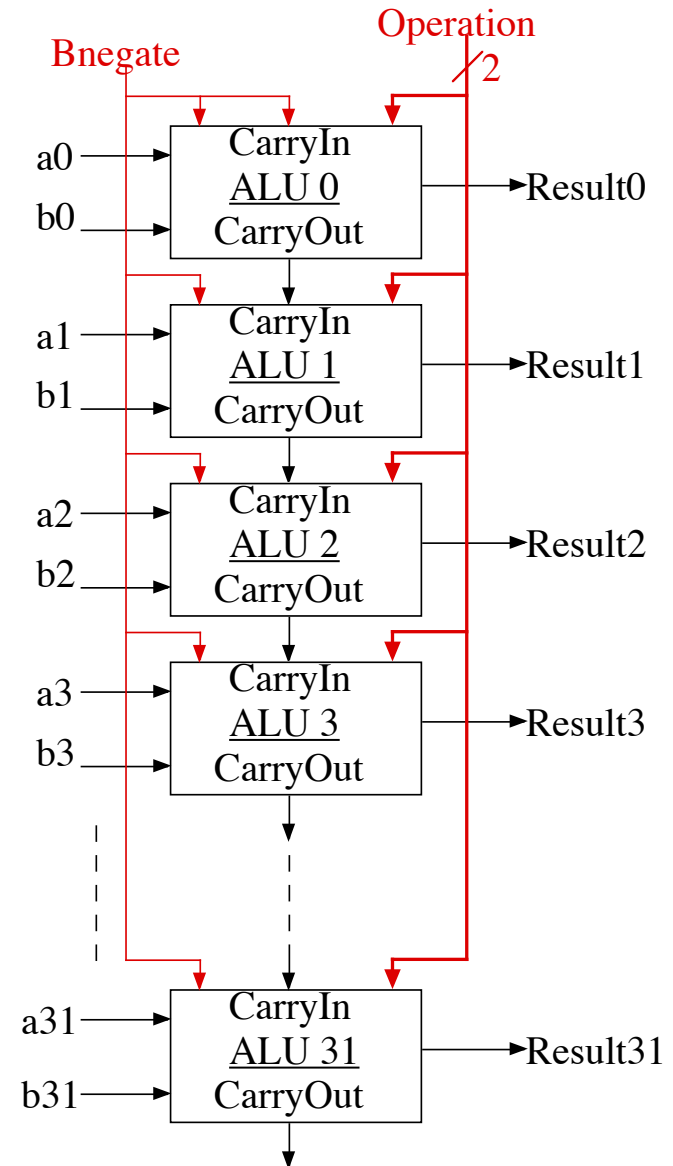

Set-less-than:

slt \$t3, \$s4, \$s7

- **slt** is an arithmetic instruction:
 - Produces 1 if **a < b**, 0 otherwise.
 - Uses subtraction: **(a - b) < 0** implies **a < b**.
 - **slt** is 1 when **(a - b)** is negative.
 - Use the sign bit to determine if **(a - b)** is negative!

- Result: bits 1 to 31 are always 0.
- Result: bit 0 is either 0 or 1.
 - But, bit 31 is the sign bit.
 - Need to connect bit 31 to bit 0.

slt \$t3, \$s4, \$s7

(\$s4 - \$s7)

if bit 31 == 1 then


\$t3 = 1 0000 0000 0000 0000 0000 0000 0000 0001

else


\$t3 = 0 0000 0000 0000 0000 0000 0000 0000 0000

Set-less-than (continued):

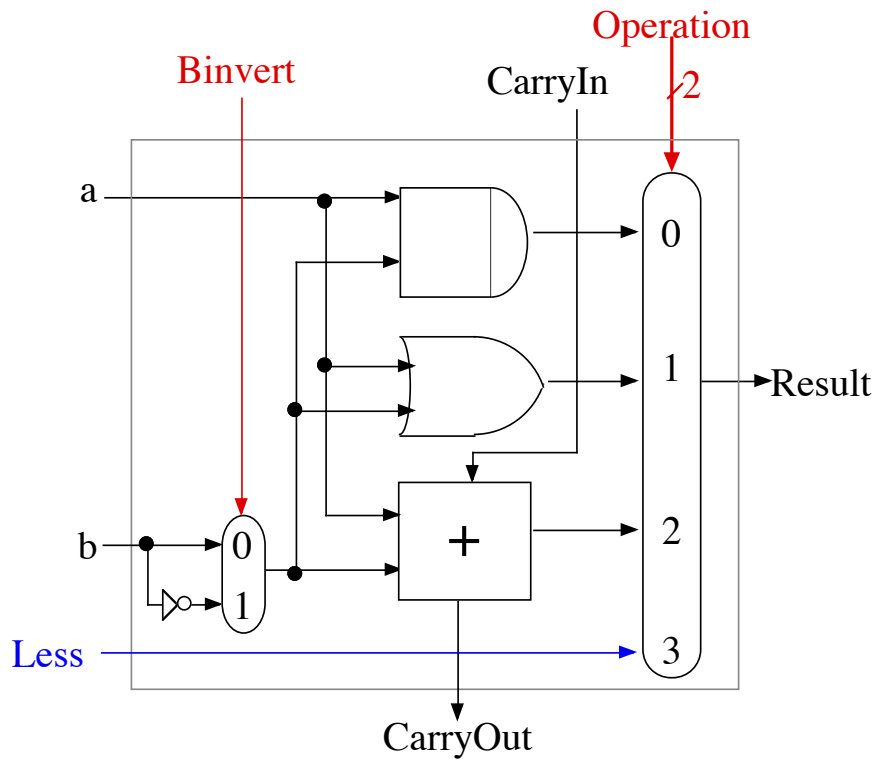31 instances of this 1-bit ALU.
Bits 0 to 30.



 
1 instance of this 1-bit ALU.
Bit 31 (most significant bit)



Set-less-than (continued):


- ALU 0 thru ALU 30 are identical units.
- ALU 31 contains overflow detection.
- The Set result for ALU 31 tells us if $(a - b) < 0$.
 - Remember: bit 31 is the sign bit.
 - Connect 0 to Less input for bits 1 to 31.
 - Connect bit 31's Set output to the Less input for bit 0.

0000 0000 0000 0000 0000 0000 0000 0001

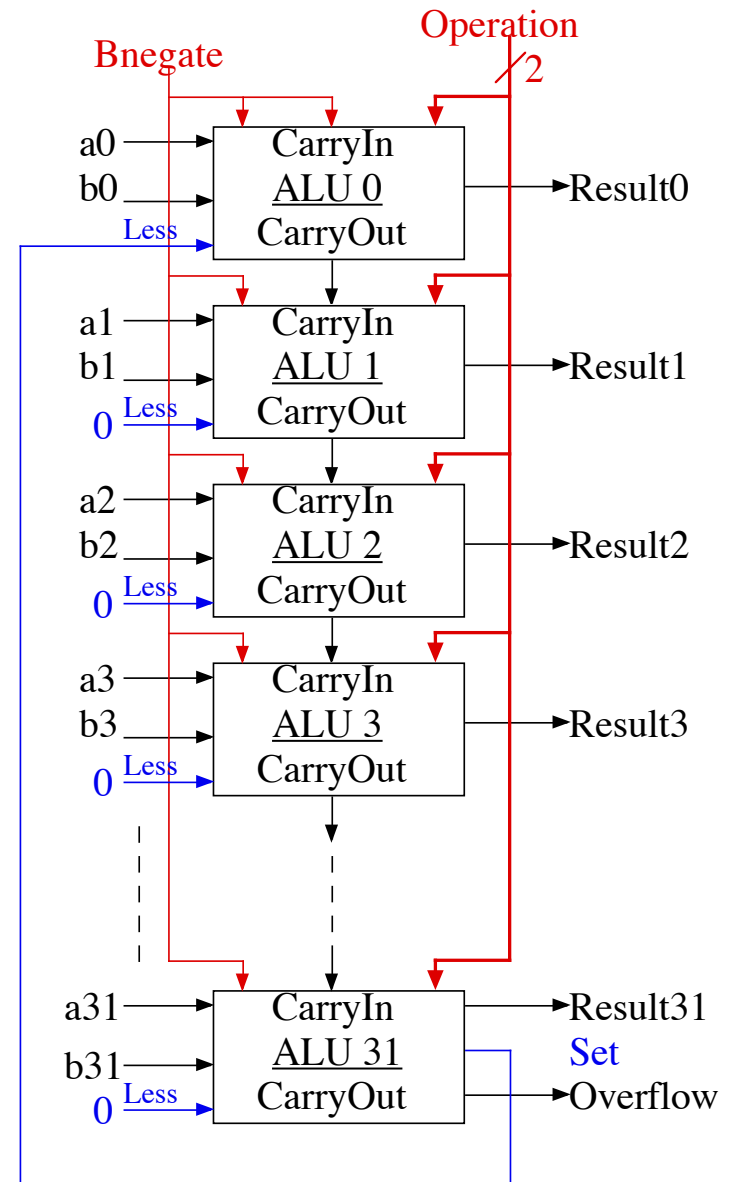

Test for Equality:

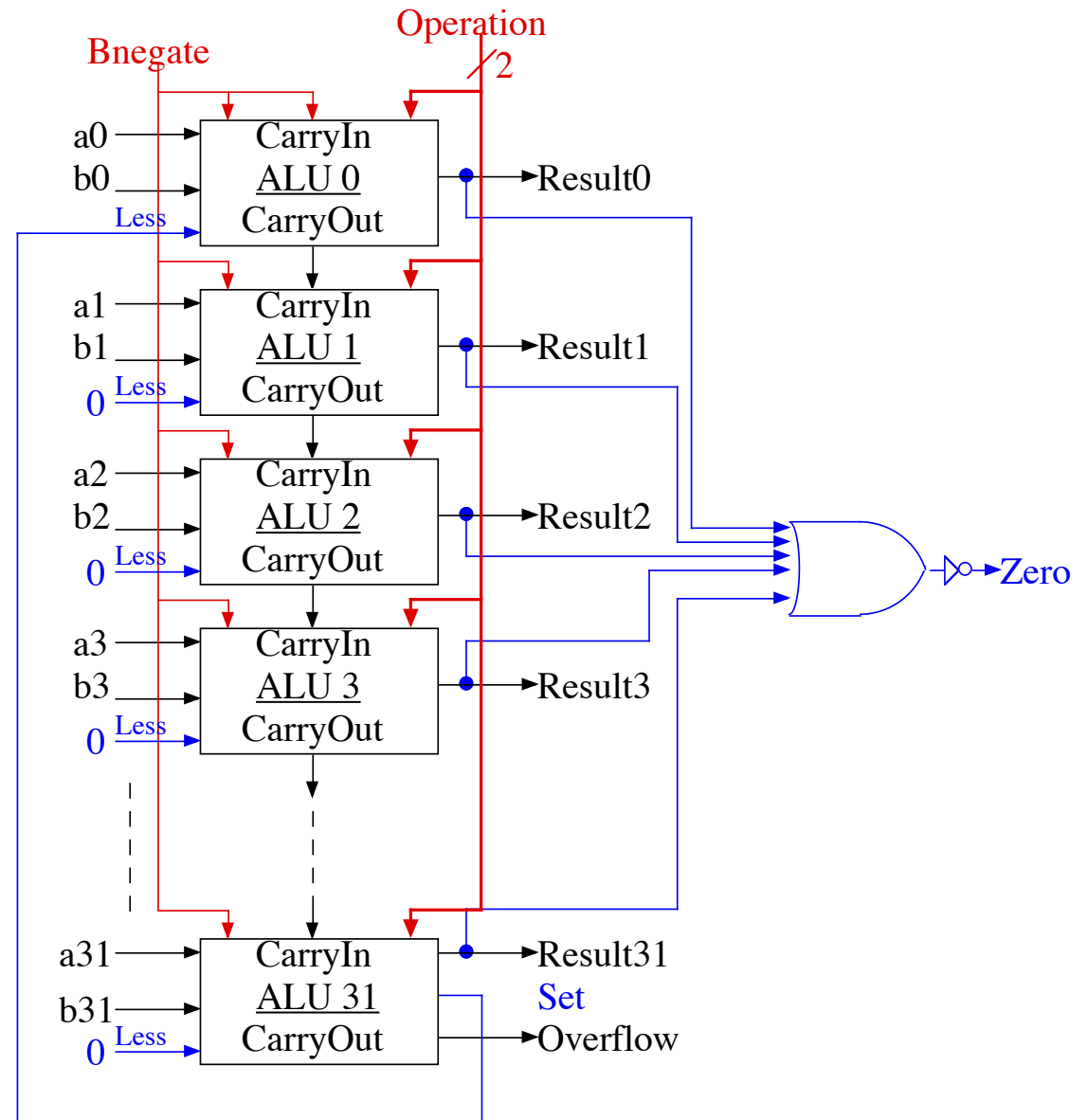- Use subtraction:
 - $(a - b) == 0$ implies $a == b$.
- Why does Zero need the NOT gate?



Control Functions for the ALU:

- Bnegate line:
 - Turned on (1) for sub, slt.
 - Turned off (0) for add, and, or.
- Operation:
 - Four functions: and, or, add, slt.
 - Add with Bnegate turned on gives subtraction.
- Five operations: add, sub, and, or, slt.
 - Three control lines:
 - Bnegate (1 line).
 - Operation (2 lines).
- Three wires can support up to 8 operations.
 - We only have 5.
 - Leaves 3 for future expansion.

ALU control lines		Function
Bnegate	Operation	
0	0 0	and
0	0 1	or
0	1 0	add
1	1 0	subtract
1	1 1	set on less than

The 3 “missing” operations: 1 00, 1 01, 0 11

ALU Summary:

- Can build an ALU to support the MIPS instruction set.
 - Key idea: Use multiplexor to select the output we want.
 - We can efficiently perform subtraction using two's complement.
 - We can replicate a 1-bit ALU to produce a 32-bit ALU.
- Important points about hardware:
 - All of the gates are always working!
 - The speed of a gate is affected by the number of inputs to the gate (fewer is faster).
 - The speed of a circuit is affected by the number of gates in series.
 - On the “critical path”, or
 - “deepest level of logic”
 - Our primary focus: Comprehension
 - However, we will take note of
 - Clever changes to organization can improve performance
 - This is similar to finding better algorithms in software.

Faster Addition: Carry Lookahead

Reading: Section C.6 (4th edition), Section B.6 (5th edition).

- Is a 32-bit ALU as fast as a 1-bit ALU?
- Is there more than one way to do addition (or to skin a cat)?
 - Two extremes: ripple carry and sum-of-products.
- What is known at the beginning of the problem?
 - $a_0, a_1, a_2, \dots, a_{31}$
 - $b_0, b_1, b_2, \dots, b_{31}$
 - c_0
 - We do not know $c_1, c_2, c_3, \dots, c_{31}$. Need to compute these.
- Basic idea: What is known, and not known, in each equation?

$$c_1 = b_0 \cdot c_0 + a_0 \cdot c_0 + a_0 \cdot b_0$$

$$c_2 = b_1 \cdot c_1 + a_1 \cdot c_1 + a_1 \cdot b_1$$

$$c_3 = b_2 \cdot c_2 + a_2 \cdot c_2 + a_2 \cdot b_2$$

$$c_4 = b_3 \cdot c_3 + a_3 \cdot c_3 + a_3 \cdot b_3$$

$$c_7 = b_6 \cdot c_6 + a_6 \cdot c_6 + a_6 \cdot b_6$$

$$\begin{array}{r} \text{????} \text{ ???} \\ 1011 \ 0111 \\ + \ 1001 \ 1101 \\ \hline \end{array}$$

Carry Lookahead (continued):

- Sum-of-products: Can you see the ripple?

$c_1 = b_0 \cdot c_0 + a_0 \cdot c_0 + a_0 \cdot b_0$ Needs 3 AND gates of 2 inputs each and a 3-input OR gate. (Total = 5 gates)

$$c_2 = b_1 \cdot c_1 + a_1 \cdot c_1 + a_1 \cdot b_1$$

$$= b_1 \cdot (b_0 \cdot c_0 + a_0 \cdot c_0 + a_0 \cdot b_0) + a_1 \cdot (b_0 \cdot c_0 + a_0 \cdot c_0 + a_0 \cdot b_0) + a_1 \cdot b_1$$

$$= b_1 \cdot b_0 \cdot c_0 + b_1 \cdot a_0 \cdot c_0 + b_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_0 \cdot c_0 + a_1 \cdot a_0 \cdot c_0 + a_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_1$$

Needs 7 AND gates of up to 3 inputs each, plus a 7-input OR gate. (Total = 19 gates)

$$c_3 = b_2 \cdot c_2 + a_2 \cdot c_2 + a_2 \cdot b_2$$

$$= b_2 \cdot (b_1 \cdot b_0 \cdot c_0 + b_1 \cdot a_0 \cdot c_0 + b_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_0 \cdot c_0 + a_1 \cdot a_0 \cdot c_0 + a_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_1) + a_2 \cdot b_2$$

$$+ a_2 \cdot (b_1 \cdot b_0 \cdot c_0 + b_1 \cdot a_0 \cdot c_0 + b_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_0 \cdot c_0 + a_1 \cdot a_0 \cdot c_0 + a_1 \cdot a_0 \cdot b_0 + a_1 \cdot b_1) + a_2 \cdot b_2$$

$$= b_2 \cdot b_1 \cdot b_0 \cdot c_0 + b_2 \cdot b_1 \cdot a_0 \cdot c_0 + b_2 \cdot b_1 \cdot a_0 \cdot b_0 + b_2 \cdot a_1 \cdot b_0 \cdot c_0 + b_2 \cdot a_1 \cdot a_0 \cdot c_0 + b_2 \cdot a_1 \cdot a_0 \cdot b_0 + b_2 \cdot a_1 \cdot b_1$$

$$+ a_2 \cdot b_1 \cdot b_0 \cdot c_0 + a_2 \cdot b_1 \cdot a_0 \cdot c_0 + a_2 \cdot b_1 \cdot a_0 \cdot b_0 + a_2 \cdot a_1 \cdot b_0 \cdot c_0 + a_2 \cdot a_1 \cdot a_0 \cdot c_0 + a_2 \cdot a_1 \cdot a_0 \cdot b_0$$

$$+ a_2 \cdot a_1 \cdot b_1 + a_2 \cdot b_2$$

Needs 15 AND gates of up to 4 inputs each, plus a 15-input OR gate. (Total = 41 + 14 = 55 gates)

$$c_4 = b_3 \cdot c_3 + a_3 \cdot c_3 + a_3 \cdot b_3$$

etc.

- Expensive! Why?

Carry Lookahead (continued):

- $$c_1 = g_0 + p_0 \cdot c_0 = a_0 \cdot b_0 + (a_0 + b_0) \cdot c_0$$

$$= a_0 \cdot b_0 + a_0 \cdot c_0 + b_0 \cdot c_0$$

Note: all of these are known at the start of the problem.

$$c_2 = g_1 + p_1 \cdot c_1 = g_1 + p_1 \cdot (g_0 + p_0 \cdot c_0)$$

$$= g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0 \quad \text{Equation A}$$

$$= a_1 \cdot b_1 + (a_1 + b_1) \cdot a_0 \cdot b_0 + (a_1 + b_1) \cdot (a_0 + b_0) \cdot c_0$$

$$= a_1 \cdot b_1 + a_1 \cdot a_0 \cdot b_0 + b_1 \cdot a_0 \cdot b_0 +$$

$$a_1 \cdot (a_0 + b_0) \cdot c_0 + b_1 \cdot (a_0 + b_0) \cdot c_0$$

$$= a_1 \cdot b_1 + a_1 \cdot a_0 \cdot b_0 + b_1 \cdot a_0 \cdot b_0 + a_1 \cdot a_0 \cdot c_0 +$$

$$a_1 \cdot b_0 \cdot c_0 + b_1 \cdot a_0 \cdot c_0 + b_1 \cdot b_0 \cdot c_0$$


7 AND gates of up to 3 inputs each.

Total number of 2-input gates:

AND gates: 13

OR gates: 6

Total: 19

 

Carry Lookahead (continued):

- It is possible to continue the sum-of-products technique.
 - But, it gets expensive -- exponential growth in the number of gates needed at each stage.
- Here is an “in-between” approach:
- Motivation:
 - If we did not know the value of carry-in, what could we do?
 - When would we always generate a carry out? $\mathbf{g_i = a_i \cdot b_i}$
 - When would we propagate the carry out? $\mathbf{p_i = a_i + b_i}$

- Example:

g:	0 0 1 0	0 0 1 0	
p:	1 0 1 1	1 1 1 1	
carry:	0 1 1 1	1 1 0 0	
a:	1 0 1 1	0 0 1 1	
b:	<u>+ 0 0 1 0</u>	<u>1 1 1 0</u>	
result:	1 1 1 0	0 0 0 1	

$\mathbf{c_2 = g_1 + p_1g_0 + p_1p_0c_0}$

$\mathbf{c_3 = g_2 + p_2g_1 + p_2p_1g_0 + p_2p_1p_0c_0}$

$\mathbf{c_4 = g_3 + p_3g_2 + p_3p_2g_1 + p_3p_2p_1g_0 + p_3p_2p_1p_0c_0}$


- $\mathbf{c_1 = g_0 + p_0 \cdot c_0 = g_0 + (a_0 + b_0)c_0}$
 $\mathbf{= a_0 \cdot b_0 + a_0 \cdot c_0 + b_0 \cdot c_0}$ Note: all of these items are known at the start of the problem.

Carry Lookahead (continued):

- But, can optimize by treating **g₀**, **p₀**, **g₁**, **p₁** as logical units.

$$\begin{aligned}c_2 &= g_1 + p_1 \cdot c_1 = g_1 + p_1 \cdot (g_0 + p_0 \cdot c_0) \\ &= g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0\end{aligned}\quad \text{Equation A}$$

 - Equation A becomes:
 - 4 AND gates:
 - two input gates: **g₀**, **g₁**, **p₁ · g₀**
 - three input gate: **p₁ · p₀ · c₀**
 - 3 OR gates:
 - two input gates: **p₀**, **p₁**
 - three input gate: **c₂**
- By comparison, the figure on the previous slide, in effect, had **g₀** twice.
 - Appears only once here.



Total number of 2-input gates:


AND gates: 5

OR gates: 4

Total: 9

Carry Lookahead (continued):

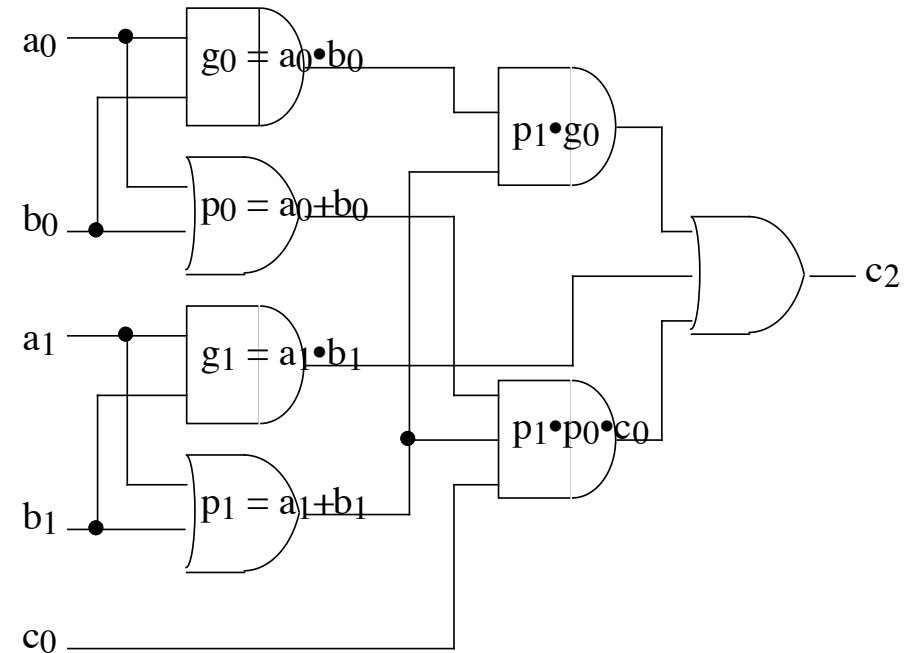- The gate count is not as many as stated by the previous slide:
Total number of 2-input gates:
AND gates: 5
OR gates: 4
Total: 9
- To implement Carry Lookahead, we only need to add:
Total number of 2-input gates:
AND gates: 3
OR gates: 2
Total: 5
- Why?




Carry Lookahead (continued):

- Continuing, we can compute c_3 :


$$\begin{aligned}c_3 &= g_2 + p_2 \cdot c_2 = g_2 + p_2 \cdot (g_1 + p_1 \cdot g_0 + p_1 \cdot p_0 \cdot c_0) \\ &= g_2 + p_2 \cdot g_1 + p_2 \cdot p_1 \cdot g_0 + p_2 \cdot p_1 \cdot p_0 \cdot c_0\end{aligned}$$

- 4 AND gates of (up to) 4 inputs each, plus 3 AND (g_0, g_1, g_2), plus 3 OR (p_0, p_1, p_2) gates of 2 inputs each.
- ditto for c_4 .
- Better!
 - More complicated than the ripple adder.
 - But, the growth in complexity is not as great as the sum-of-products approach.
 - Compromise between performance and complexity.
- Called a *Carry Lookahead Adder*, or CLA.
- There is a practical limit to the number of inputs to a CLA.
 - We will assume 4-bits.

 

“Super” Carry Lookahead:

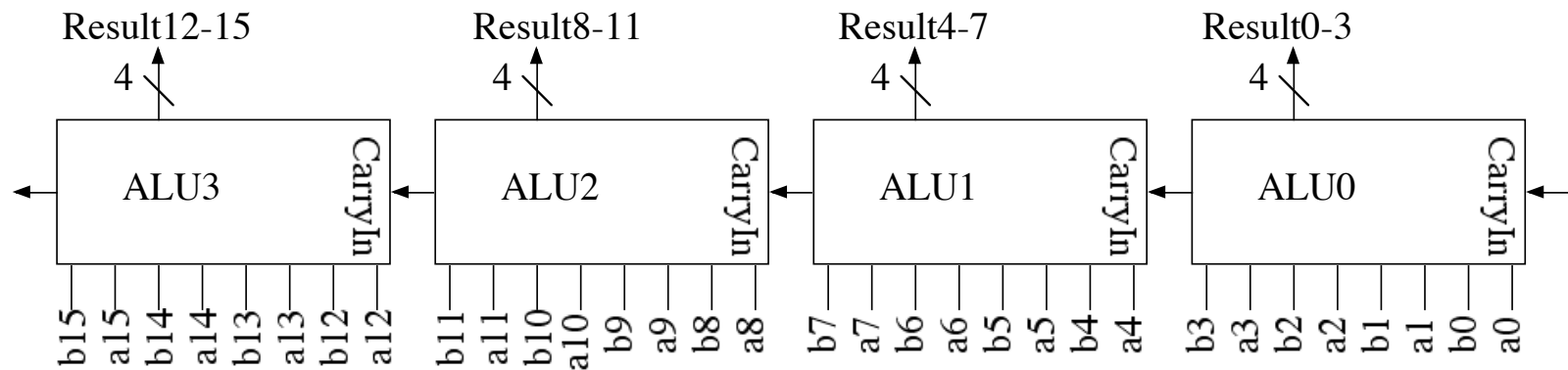- Another level of abstraction is needed:
- Consider a 16-bit adder, constructed using 4-bit CLA's.
 - Use 4 CLA's to handle adding the 16-bit values 4 bits at a time.
 - Need to compute the carry from one 4-bit CLA to the next.
 - Could do this using a ripple add.
 - An improvement over the original ripple adder (why?).
 - We can do better.



“Super” Carry Lookahead (continued):

- “Super” bits to the rescue!
- Compute “super” propagate bits:
- Compute “super” generate bits:

$$P0 = p_3 \cdot p_2 \cdot p_1 \cdot p_0$$

$$P1 = p_7 \cdot p_6 \cdot p_5 \cdot p_4$$

$$P2 = p_{11} \cdot p_{10} \cdot p_9 \cdot p_8$$


$$P3 = p_{15} \cdot p_{14} \cdot p_{13} \cdot p_{12}$$

$$G0 = g_3 + p_3 \cdot g_2 + p_3 \cdot p_2 \cdot g_1 + p_3 \cdot p_2 \cdot p_1 \cdot g_0$$

$$G1 = g_7 + p_7 \cdot g_6 + p_7 \cdot p_6 \cdot g_5 + p_7 \cdot p_6 \cdot p_5 \cdot g_4$$

$$G2 = g_{11} + p_{11} \cdot g_{10} + p_{11} \cdot p_{10} \cdot g_9 + p_{11} \cdot p_{10} \cdot p_9 \cdot g_8$$
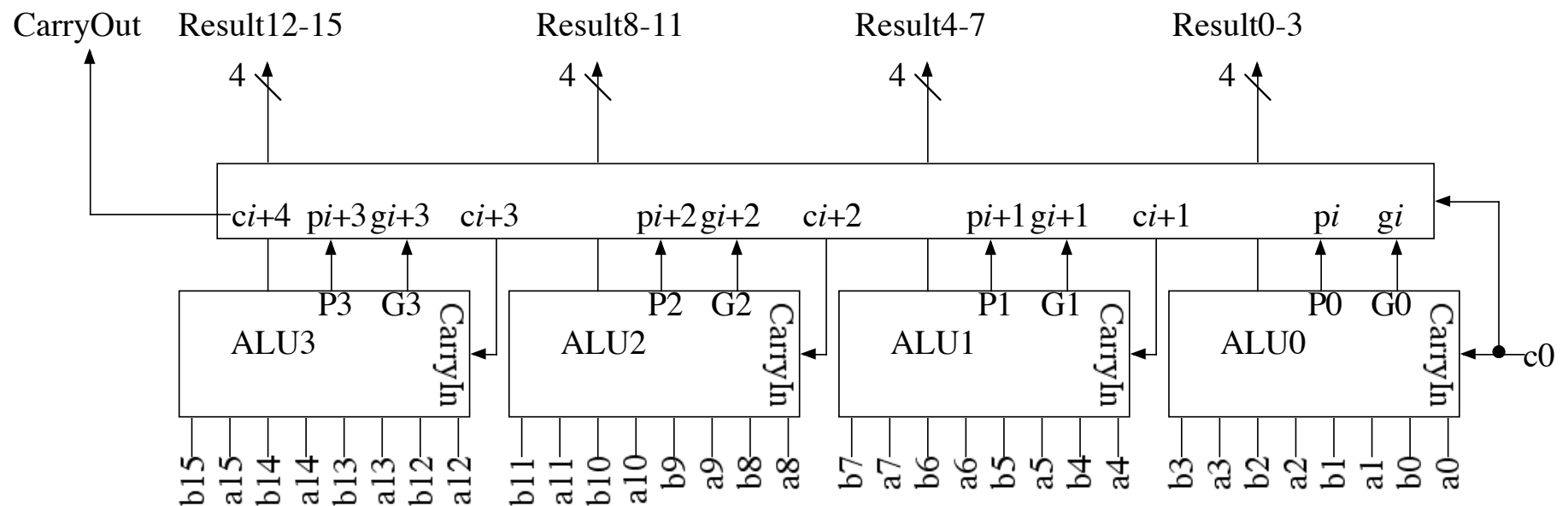
$$G3 = g_{15} + p_{15} \cdot g_{14} + p_{15} \cdot p_{14} \cdot g_{13} + p_{15} \cdot p_{14} \cdot p_{13} \cdot g_{12}$$



“Super” Carry Lookahead (continued):

- Example from pages C-44 to C-46 (4th edition):
- Determine the **gi**, **pi**, **Pi**, and **Gi** values of these two 16-bit numbers:

a: 0001 1010 0011 0011_{two}

b: 1110 0101 1110 1011_{two}

Also, what is **CarryOut15 (C4)**?

- Solution:

a: 0001 1010 0011 0011

b: 1110 0101 1110 1011

gi: 0000 0000 0010 0011 determined from $a_i \cdot b_i$

pi: 1111 1111 1111 1011 determined from $a_i + b_i$

- Compute the “super” propagates:

$$P0 = p3 \cdot p2 \cdot p1 \cdot p0 = 1 \cdot 0 \cdot 1 \cdot 1 = 0$$

$$P1 = p7 \cdot p6 \cdot p5 \cdot p4 = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

$$P2 = p11 \cdot p10 \cdot p9 \cdot p8 = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

$$P3 = p15 \cdot p14 \cdot p13 \cdot p12 = 1 \cdot 1 \cdot 1 \cdot 1 = 1$$

- Compute the “super” generates:

$$G0 = g3 + p3 \cdot g2 + p3 \cdot p2 \cdot g1 + p3 \cdot p2 \cdot p1 \cdot g0 = 0 + 1 \cdot 0 + 1 \cdot 0 \cdot 1 + 1 \cdot 0 \cdot 1 \cdot 1 = 0 + 0 + 0 + 0 = 0$$

$$G1 = g7 + p7 \cdot g6 + p7 \cdot p6 \cdot g5 + p7 \cdot p6 \cdot p5 \cdot g4 = 0 + 1 \cdot 0 + 1 \cdot 1 \cdot 1 + 1 \cdot 1 \cdot 1 \cdot 0 = 0 + 0 + 1 + 0 = 1$$

$$G2 = g11 + p11 \cdot g10 + p11 \cdot p10 \cdot g9 + p11 \cdot p10 \cdot p9 \cdot g8 = 0 + 1 \cdot 0 + 1 \cdot 1 \cdot 0 + 1 \cdot 1 \cdot 1 \cdot 0 = 0 + 0 + 0 + 0 = 0$$

$$G3 = g15 + p15 \cdot g14 + p15 \cdot p14 \cdot g13 + p15 \cdot p14 \cdot p13 \cdot g12 = 0 + 1 \cdot 0 + 1 \cdot 1 \cdot 0 + 1 \cdot 1 \cdot 1 \cdot 0 = 0 + 0 + 0 + 0 = 0$$

“Super” Carry Lookahead (continued):

- From the previous slide:

$$\begin{array}{llll} \mathbf{P0} = \mathbf{0} & \mathbf{P1} = \mathbf{1} & \mathbf{P2} = \mathbf{1} & \mathbf{P3} = \mathbf{1} \\ \mathbf{G0} = \mathbf{0} & \mathbf{G1} = \mathbf{1} & \mathbf{G2} = \mathbf{0} & \mathbf{G3} = \mathbf{0} \end{array}$$

- Which gives:

$$\begin{array}{llllll} \mathbf{C1} & = & \mathbf{G0} & + & \mathbf{P0} \cdot \mathbf{c0} & \\ & = & \mathbf{0} & + & \mathbf{0} \cdot \mathbf{0} & \\ & = & \mathbf{0} & + & \mathbf{0} & = \mathbf{0} = \mathbf{C1} \\ \mathbf{C2} & = & \mathbf{G1} & + & \mathbf{P1} \cdot \mathbf{G0} & + & \mathbf{P1} \cdot \mathbf{P0} \cdot \mathbf{c0} \\ & = & \mathbf{1} & + & \mathbf{1} \cdot \mathbf{0} & + & \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{0} \\ & = & \mathbf{1} & + & \mathbf{0} & + & \mathbf{0} & = \mathbf{1} = \mathbf{C2} \\ \mathbf{C3} & = & \mathbf{G2} & + & \mathbf{P2} \cdot \mathbf{G1} & + & \mathbf{P2} \cdot \mathbf{P1} \cdot \mathbf{G0} & + & \mathbf{P2} \cdot \mathbf{P1} \cdot \mathbf{P0} \cdot \mathbf{c0} \\ & = & \mathbf{0} & + & \mathbf{1} \cdot \mathbf{1} & + & \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{0} & + & \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{0} \cdot \mathbf{0} \\ & = & \mathbf{0} & + & \mathbf{1} & + & \mathbf{0} & + & \mathbf{0} & = \mathbf{1} = \mathbf{C3} \\ \mathbf{C4} & = & \mathbf{G3} & + & \mathbf{P3} \cdot \mathbf{G2} & + & \mathbf{P3} \cdot \mathbf{P2} \cdot \mathbf{G1} & + & \mathbf{P3} \cdot \mathbf{P2} \cdot \mathbf{P1} \cdot \mathbf{G0} & + & \mathbf{P3} \cdot \mathbf{P2} \cdot \mathbf{P1} \cdot \mathbf{P0} \cdot \mathbf{c0} \\ & = & \mathbf{0} & + & \mathbf{1} \cdot \mathbf{0} & + & \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{1} & + & \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{0} & + & \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{1} \cdot \mathbf{0} \cdot \mathbf{0} \\ & = & \mathbf{0} & + & \mathbf{0} & + & \mathbf{1} & + & \mathbf{0} & + & \mathbf{0} & = \mathbf{1} = \mathbf{C4} \end{array}$$

- Note: All of the C's can be calculated at the same time!
- The sequence then becomes:
 - Calculate all of the **P's** and **G's** at the same time.
 - Calculate all of the **C's** at the same time. Now, the carry-in to each CLA is known.
 - Calculate all of the result bits at the same time.

“Super” Carry Lookahead (continued):

0110 1001 1110 0010
+ 1001 1011 0100 0011

p 1111 1011 1110 0011

g 0000 1001 0100 0010

P 1 0 0 0

G 0 1 1 0

1 1 1 0

The carry-in to each 4-bit adder

0110 1001 1110 0010
+ 1001 1011 0100 0011

“Super” Carry Lookahead (continued):

- Suppose we don’t know the bits of the two numbers, but we do know all the **p** and **g** bits:

xxxx xxxx xxxx xxxx

? xxxx xxxx xxxx xxxx

p 1111 1011 1110 0011

g 0000 1001 0100 0010

P 1 0 0 0

G 0 1 1 0

1 1111 111 1 0 1??

xxxx 10x1 x1x0 001x

- xxxx 10x1 x1x0 001x

0000 0101 0010 01??

0000 0101 0010 0101 addition, no overflow

0000 0101 0010 0110 subtraction, maybe overflow, maybe not

Multiplication


Reading: Section 3.3: pages 230-236 (4th edition), pages 183-188 (5th edition).

- More complicated than addition.
 - Accomplished with shifting and addition.
- Takes more time and requires more area on the CPU (that is, more transistors).
- Will look at 3 versions, all based on the grade school multiplication algorithm:

```
      01100111
    * 01001101
    -----
      01100111
      00000000
      01100111
      01100111
      00000000
      00000000
      01100111
      00000000
    -----
    000111101111011
```

Multiplication (continued):

- Version One:

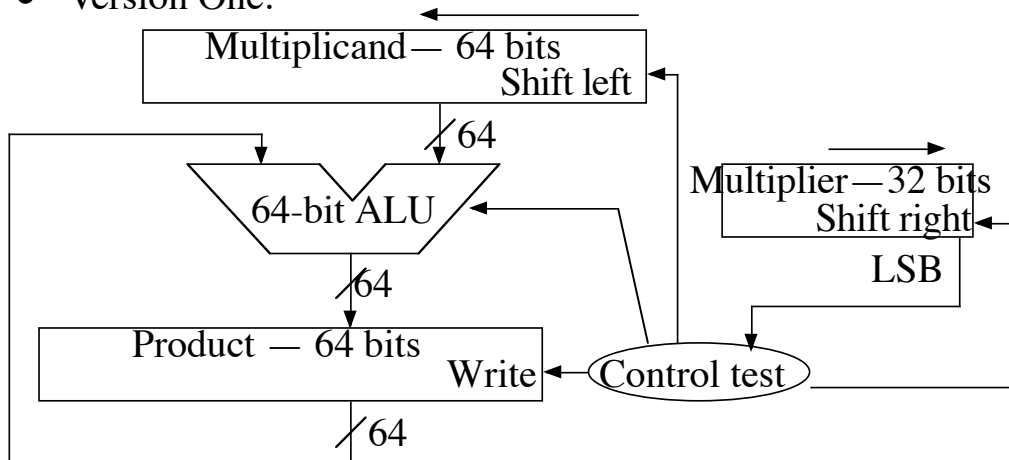

- Multiplicand:


- Stored in right half (right 32-bits) of register.
- Shifted left one bit on each iteration.

- Multiplier:

- Shifted right one bit.
- Look at least-significant bit only on each iteration.


- Product:

- Potentially a 64-bit answer.

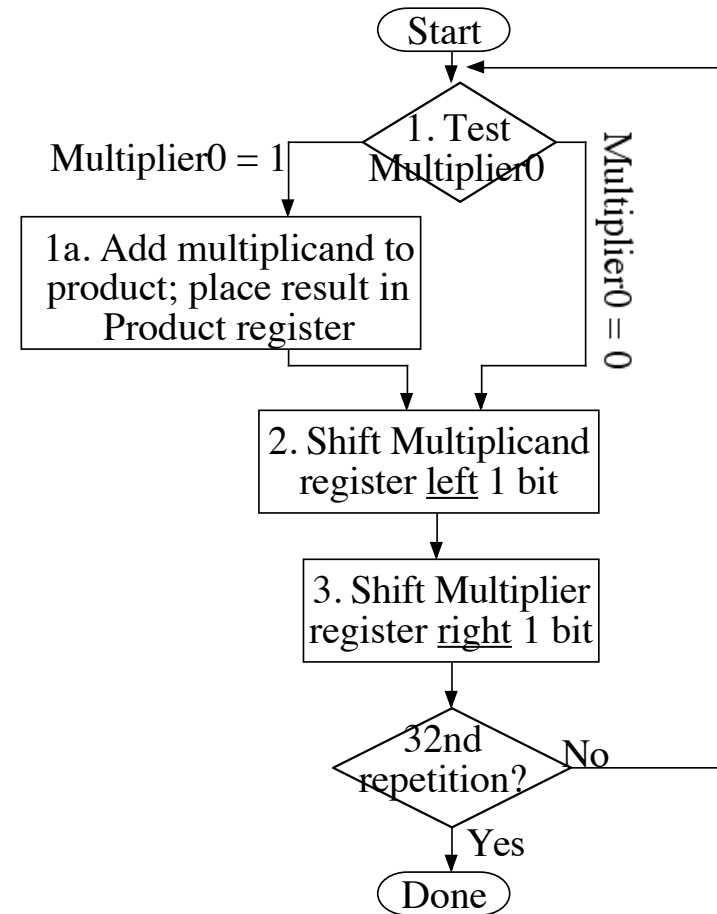


Multiplication (continued):


- Version Two:

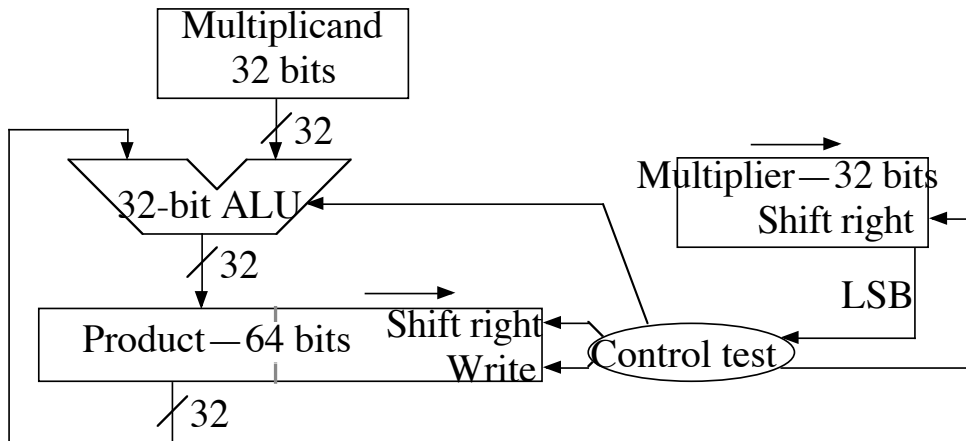

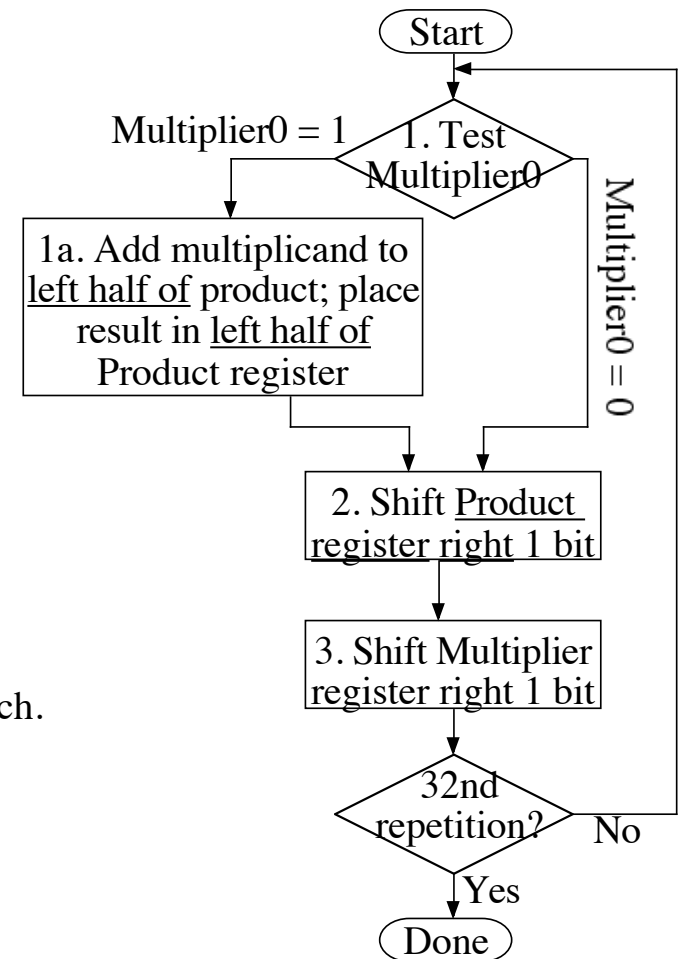
- Multiplicand register, ALU, and Multiplier register are now 32-bits each.
- Product is now shifted right.



Multiplication (continued):

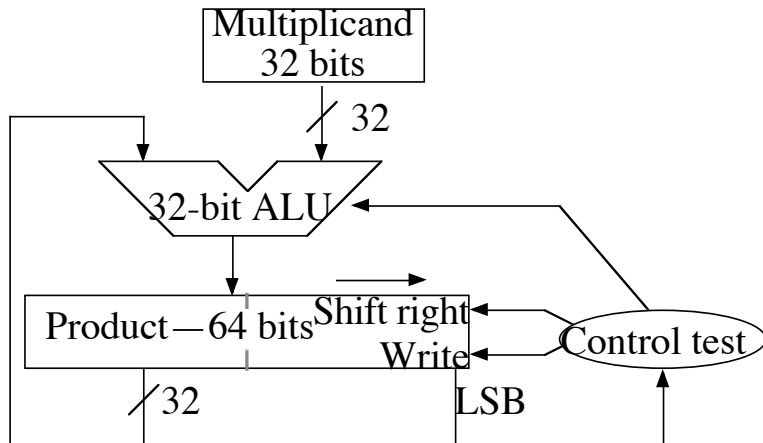

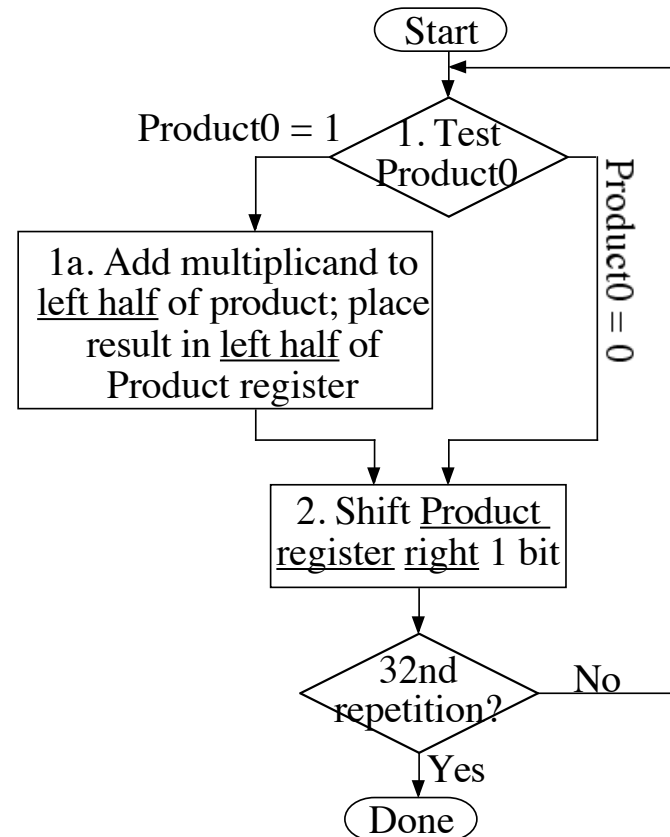- Separate Multiplier register is gone.
- Put Multiplier initially in the right-half of the product register.
 - As the product is computed and shifted right, the multiplier will shift right as well.
 - Right-most bit (LSB) of Product register is the bit tested in the first if.
 - Step 3 is gone.



Multiplication in MIPS:

Reading: Spim Appendix, page 53.

- Two versions:
 - Signed multiplication: **mult**
mult \$s1, \$s2 # multiply signed \$s1 * \$s2
 - Unsigned multiplication: **multu**
multu \$s3, \$s4 # multiply unsigned \$s3 * \$s4
- Note: No destination register!!
 - The product goes into two special-purpose registers (not part of the 32 general-purpose registers).
 - **lo** holds the lower 32-bits of the product.
 - **hi** holds the upper 32-bits of the product.
 - Use **mflo** (move from **lo**) and **mfhi** (move from **hi**)
mflo \$s1 # move 32 bit value from lo to \$s1
mfhi \$s2 # move 32 bit value from hi to \$s2
- Notes:
 - The programmer (that would be you!) must test for overflow — not done by **mult**.
 - Pseudo-instructions are available in MIPS that specify a destination register: **mul**, **multo**, **mulou**.

Division:

- Will skip Section 3.4 (4th and 5th editions), Division.
- But, take note of MIPS division instructions:
 - “Divide in MIPS”
 - Pages 241-242 (4th edition).
 - Page 52 in Spim Appendix: **div**, **divu** instructions.
- Analogous to multiply.
- Register **lo** holds the quotient.
- Register **hi** holds the remainder.

Summary:

- Computer arithmetic is constrained by limited precision.
 - Limited range of values for integers and floating-point.
 - Floating-point further limited by fractional part.
- Bit patterns have no inherent meaning but standards do exist.
 - Two's complement.
 - IEEE 754 floating-point.
- Computer instructions determine “meaning” of the bit patterns.
- Performance and accuracy are important; thus, there are many complexities in real machines.
- Basics of Gates and Boolean Algebra.
- Basics of integer ALU.