


# The Processor

Read: Section 4.1, pages 300-303 (4th edition)

- We are ready to look at an implementation of the MIPS CPU.
- Simplified to contain only:
  - Memory-reference instructions: **lw**, **sw**.
  - Arithmetic-logical instructions: **add**, **sub**, **and**, **or**, **slt**.
  - Control flow instructions: **beq**, **j**.
- Generic implementation:
  - Use the Program Counter (PC) to supply the instruction address.
  - Get the instruction from memory.
  - Read values from registers.
  - Use the instruction to decide exactly what to do.
- All instructions (except **j**) use the ALU after reading the registers.
  - Why? Memory-reference? Arithmetic? Control flow?

## Implementation Overview:


- Abstract/Simplified View:

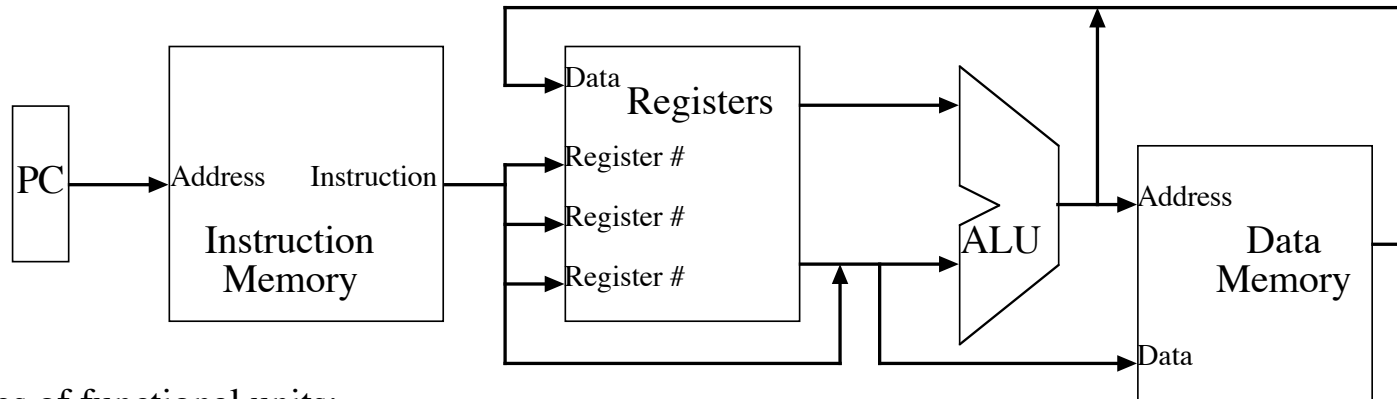


- Two types of functional units:
  - Elements that operate on data values (*combinational* units).
    - Outputs depend only on the current inputs.
    - Example: ALU
  - Elements that contain state (*sequential* units).
    - Has some internal storage (*state*).
    - Example: instruction memory and data memory.
    - Example: registers.
 
### Implementation Overview (continued):

- State Elements:
  - Reading: Section 4.2, pages 303-307 (4th edition)
- Unclocked vs. Clocked: when do we read values, when do we write them?
- Clocks used in synchronous logic:
  - When should an element that contains state be updated?




 - Do not want to update and read at the same time, since state may be inconsistent.


 
### Implementation Overview (continued):


- Clocking Methodology:
  - Will assume “edge-triggered”
    - Still completes in one clock cycle.
    - No feedback can occur in this design — chapter 4 designs fit this requirement.
  - Assume a “simple” implementation:
    - A single long clock cycle is used for every instruction.
    - Easier to understand (yea!).
  - Not practical:
    - Want different instruction classes to take different numbers of clock cycles
      - Improves overall performance.
      - Each clock cycle is then much shorter.
      - More realistic.
      - Requires more complex control.


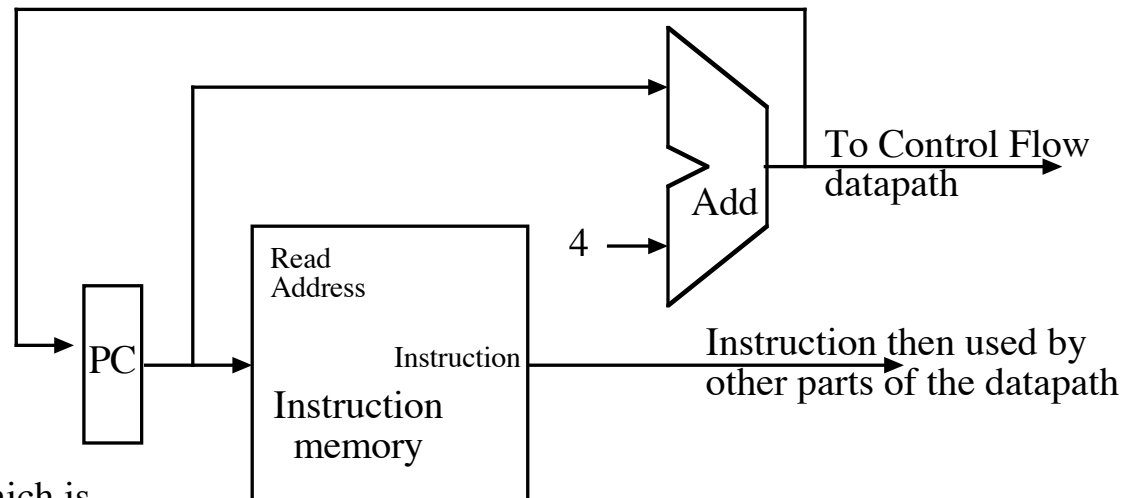
### **Building a datapath:**

- Used by all three classes of instructions.
  - J-format, R-format, I-format.
- Instruction memory:
  - State unit, holds the instructions that make up the program.
  - Given an address, produces an instruction (four bytes).
- Program Counter, PC:
  - State unit.
  - Holds address of the *next* instruction.
- Add ALU:
  - Combinational unit.
  - Hard-wired to perform only addition.
  - Always uses 4 as the second operand, which is the size (in bytes) of one instruction.


- Reading: Section 4.3, pages 307- (4th edition)



# sub \$t7, \$s2, \$s3
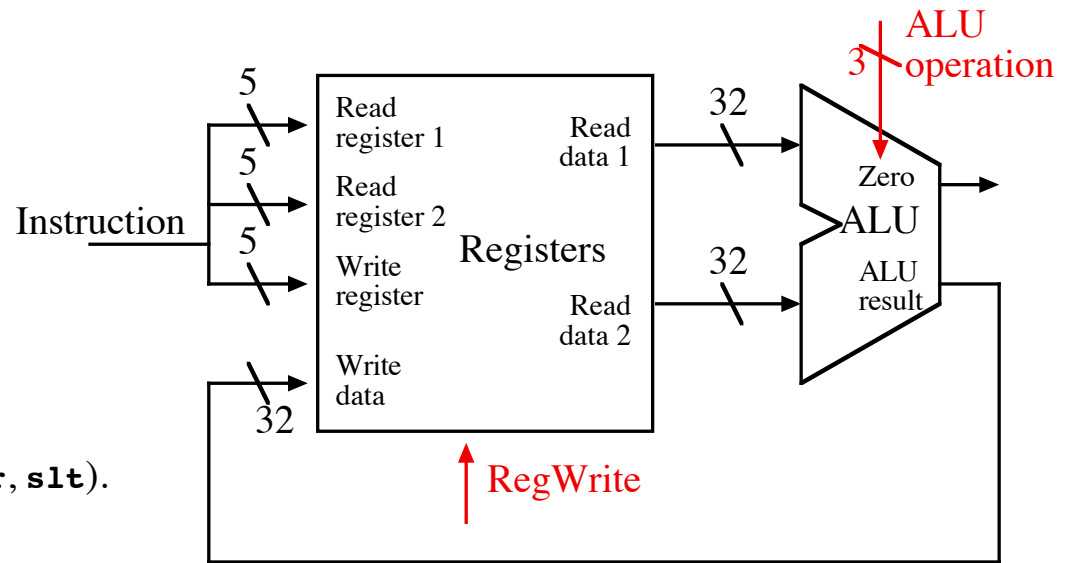
## Building a Datapath (continued):

- R-format Instructions:
  - **add, sub, and, or, slt.**
  - Three register operands needed.
  - Read two data words from the register file.
  - Write one data word into the register file.
- **ALU** is the full-featured ALU (see Appendix B):
  - 3 control bits for ALU operations:
    - 2 to specify the Operations (**add, and, or, slt**).
    - 1 for Bnegate (used for **sub, slt**).



- **Registers** inputs and outputs:
 


31							0
R	op	rs	rt	rd	shamt	funct	


  - Four inputs:
    - 3 register numbers (5 bits each).
    - 1 register value for writing the result (32 bits).
  - Two outputs:
    - 2 register values for ALU (32 bits each).
  - Control
    - 1 control value asserted to write a value to a register.
    - (Register file always outputs the contents of register numbers indicated on the Read register inputs.)

# Building a Datapath (continued):

I	op	rs	rt	16 bit number	
	6 bits	5 bits	5 bits	5 bits	6 bits

- Memory-reference instructions: **lw**, **sw**
  - Example: **lw \$t1, offset\_value(\$t2)**
  - Get contents of data memory at **\$t2 + offset\_value** and place in register **\$t1**.
- Sign extend unit: the **offset\_value** is a 16-bit signed value. Must convert (“extend”) to a 32-bit signed value.
- Memory unit: Address gives location. Can read value (output) or write value (input).
  - Two inputs: address and write data (both 32 bits).
  - One output: read Data (32 bits).
  - Two control wires: **MemWrite**, **MemRead**.

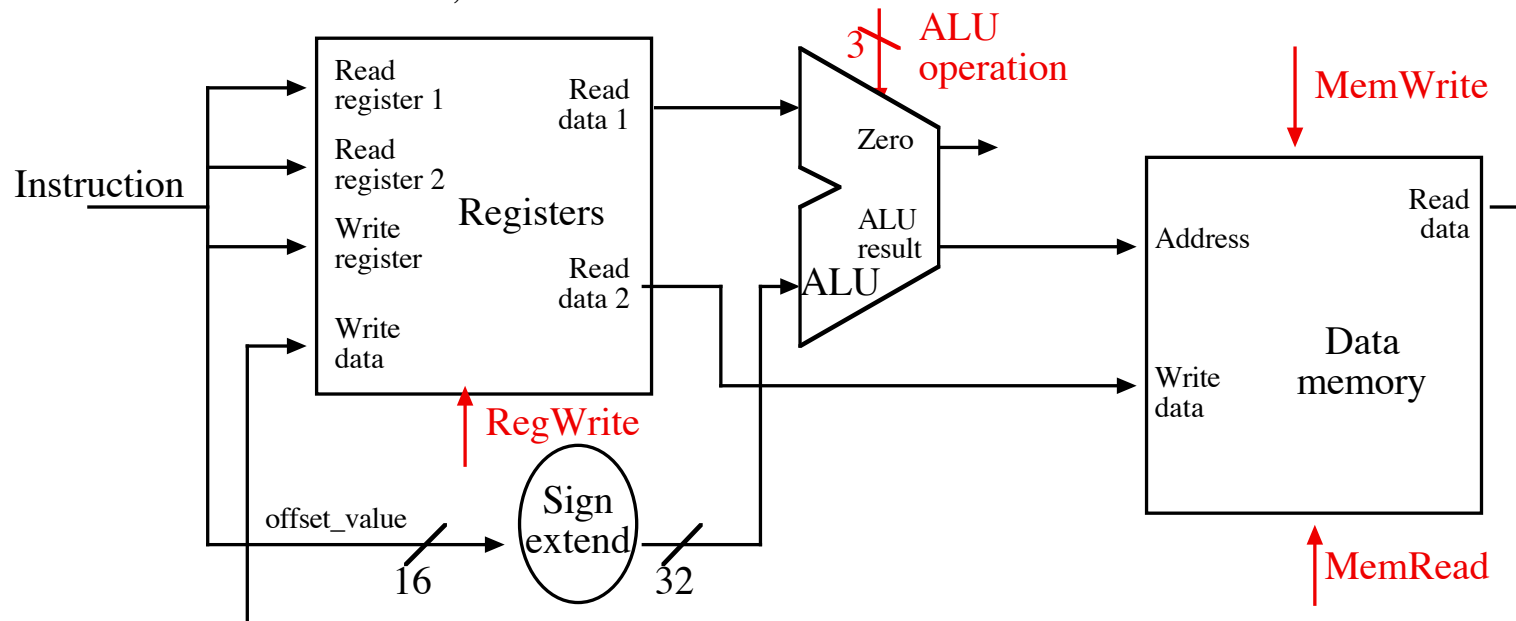


 

### Building a Datapath (continued):

- Implementing Control Flow Instructions:
  - **beq**: 3 operands; 2 registers to compare, and a 16-bit signed offset from the PC.
  - Base address is the address of the instruction *following* the current instructions.
  - Offset is shifted two places (all instruction addresses are *word-aligned*).
  - Two outputs: Result of comparison, and Branch target.


```
beq    $t2, $s7, atTheEnd
```

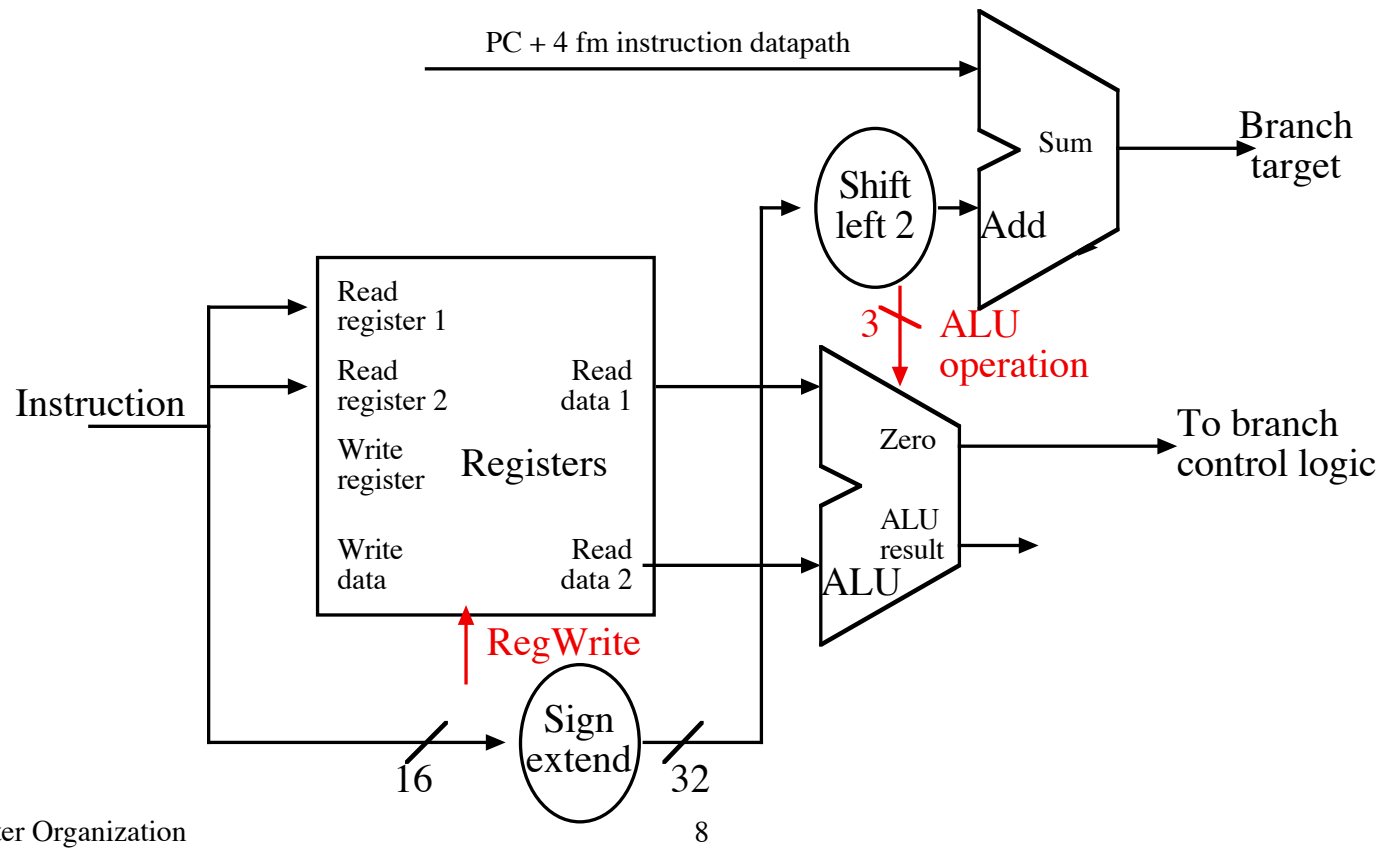



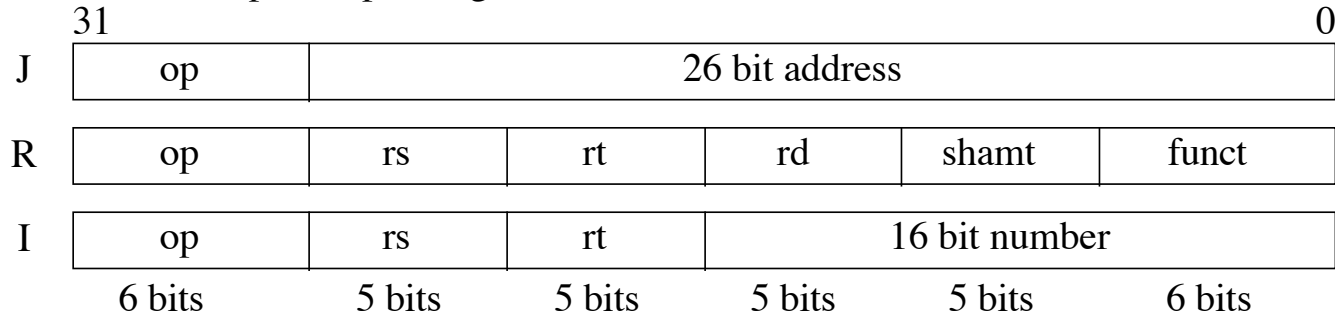
### Single-cycle Implementation:

- Reading: Section 4.4, pages 316-330 (4th edition)
- Single Datapath from the four pieces shown earlier (and described in Section 4.2).
  - Memory-reference instructions: **lw**, **sw**.
  - Arithmetic-logical instructions: **add**, **sub**, **and**, **or**, **slt**.
  - Control flow instructions: **beq**, **j**.
- Simplest datapath: execute each instruction in a single clock cycle.
- Requires some duplication of elements (multiple ALU's, for example).
- Requires separate instruction memory and data memory.
- Can share some elements from different datapaths.
  - Multiplexors are necessary several places.
  - Choose between two inputs depending on the instruction.



## Implementation Overview:

- Abstract/Simplified View:

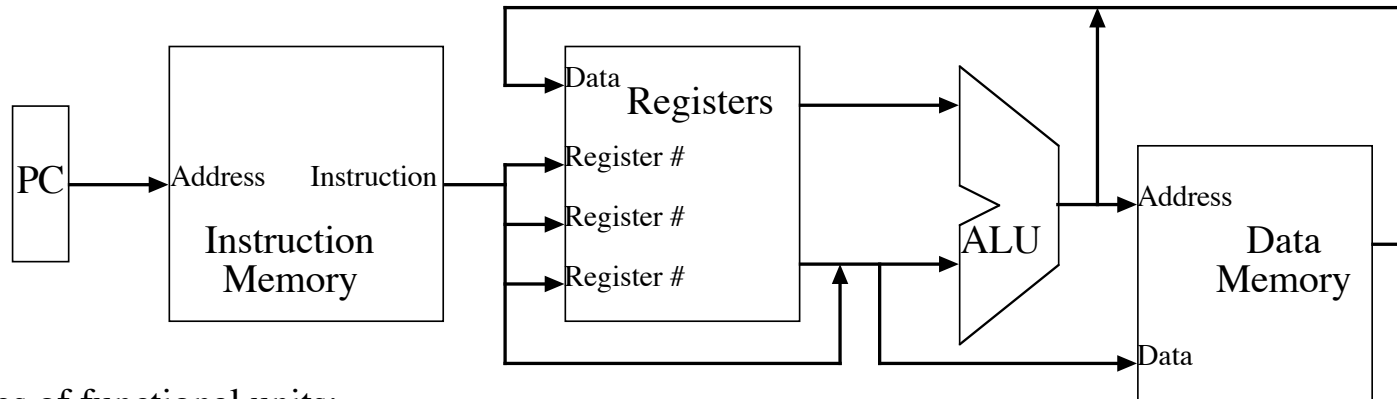

- Two types of functional units:
  - Elements that operate on data values (*combinational* units).
    - Outputs depend only on the current inputs.
    - Example: ALU
  - Elements that contain state (*sequential* units).
    - Has some internal storage (*state*).
    - Example: instruction memory and data memory.
    - Example: registers.

- Overview:




R

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------
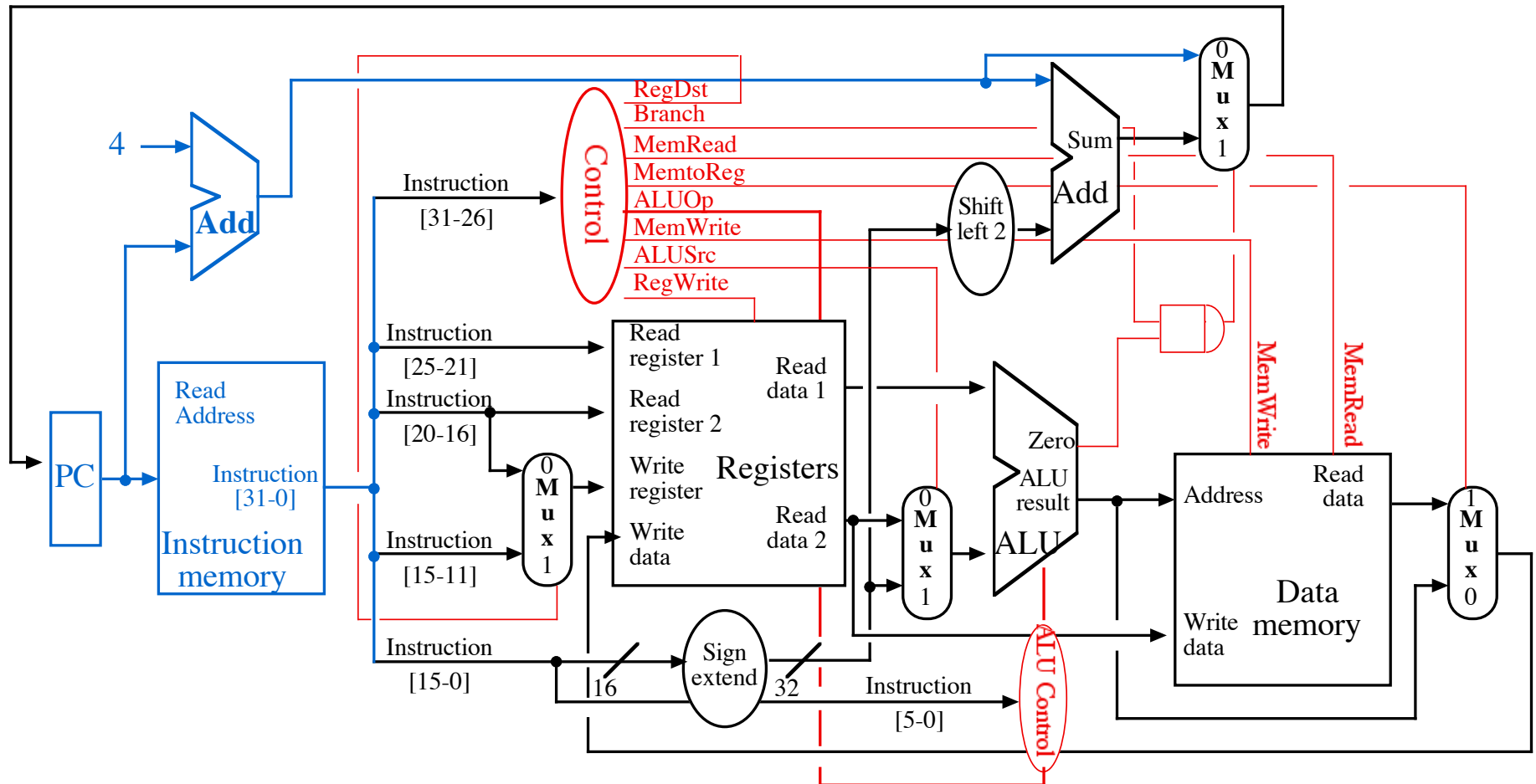
### Single-cycle Implementation (continued):

- R-Format instruction: **add**, **sub**, **slt**, **and**, **or**.
- Fetch: Get instruction from memory and increment PC.


Blue lines/text indicate the current action.




R	op	rs	rt	rd	shamt	funct
---	----	----	----	----	-------	-------
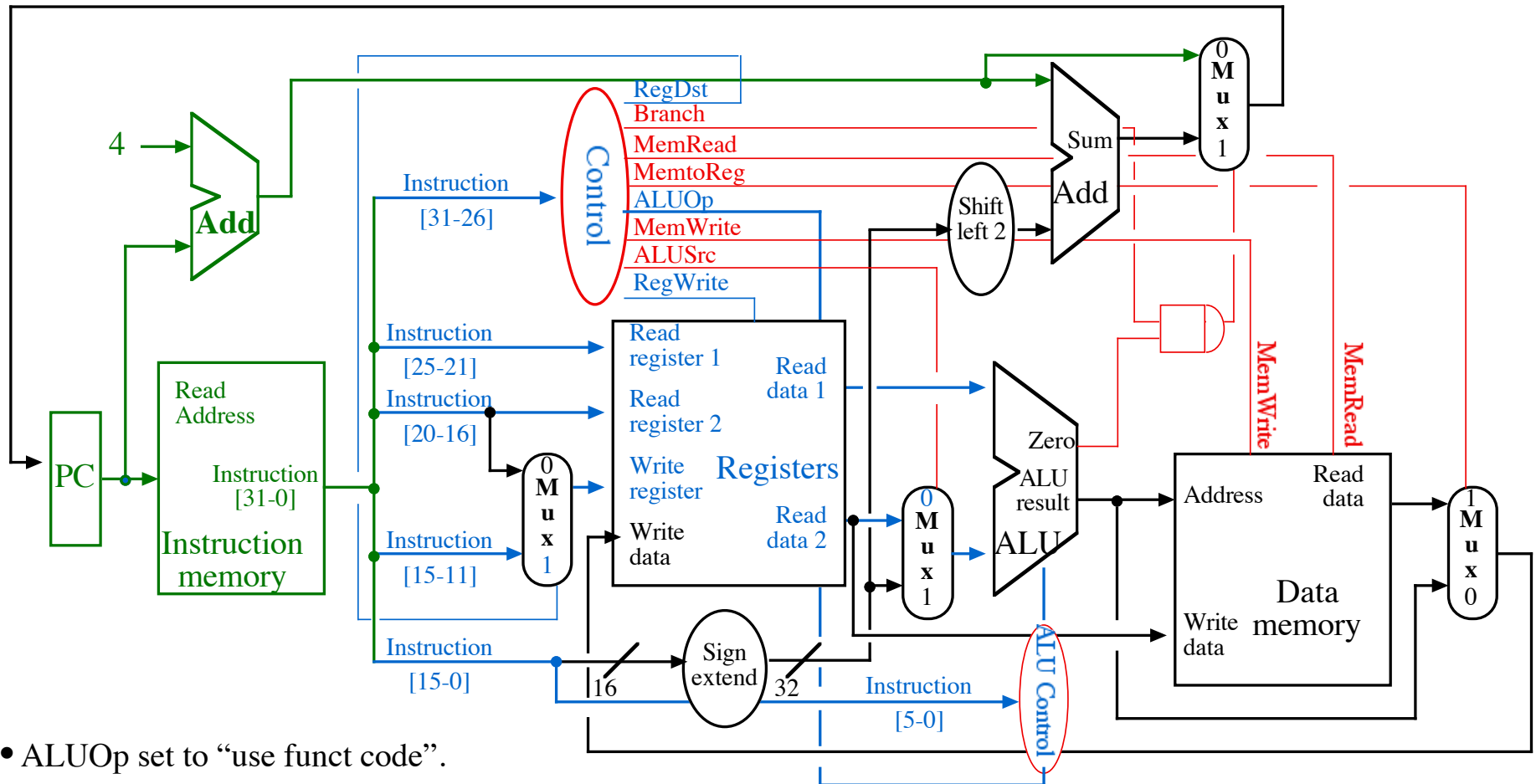
### Single-cycle Implementation (continued):


- R-Format instruction: Get the two source register values from Register file.
- Indicate register to write (will be written later).
- RegDst and RegWrite turned on.



 
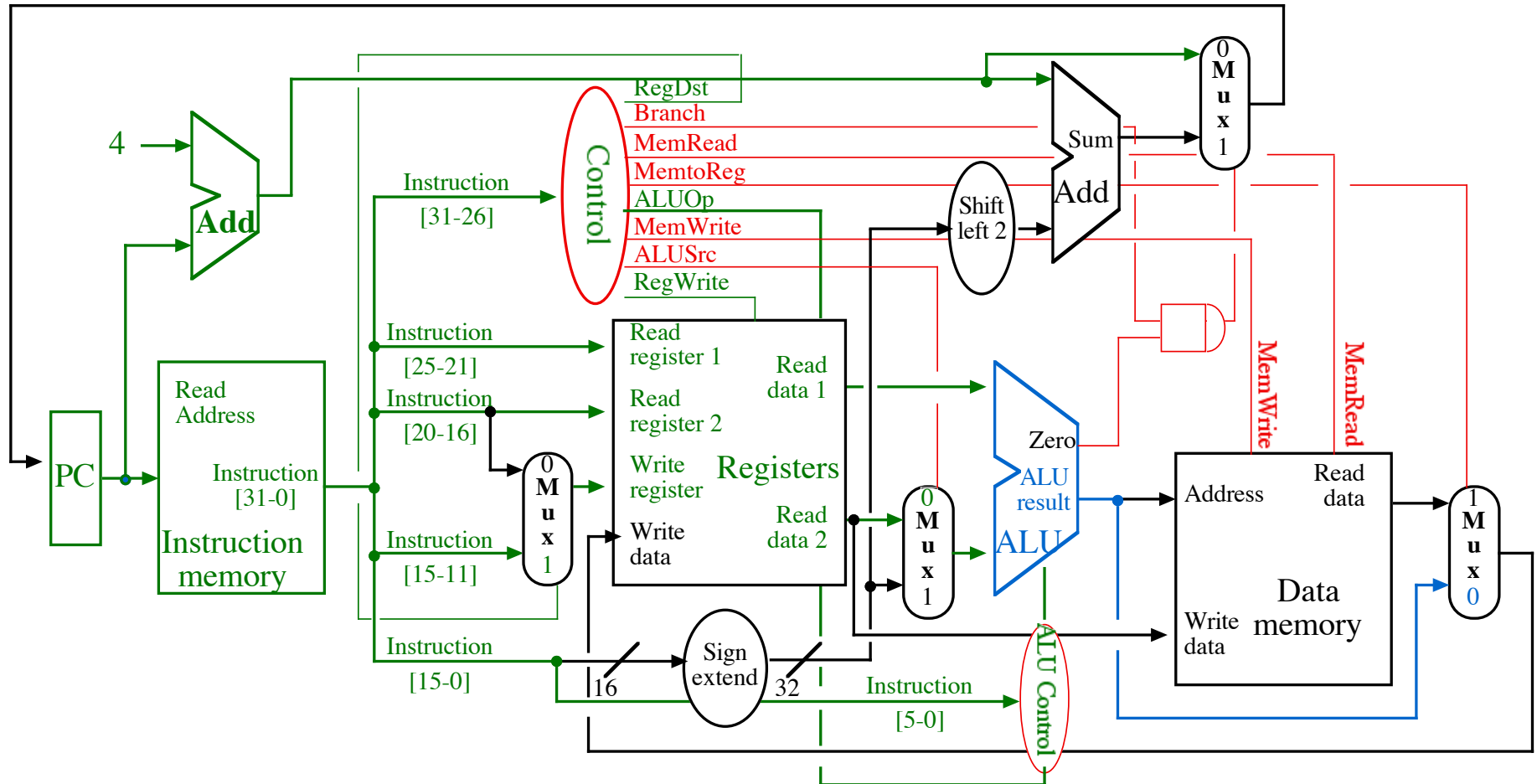
### Single-cycle Implementation (continued):

- R-Format instruction: Compute the answer.
- MemtoReg is 0; we want the ALU result to go to the Registers.




R

op	rs	rt	rd	shamt	funct
----	----	----	----	-------	-------
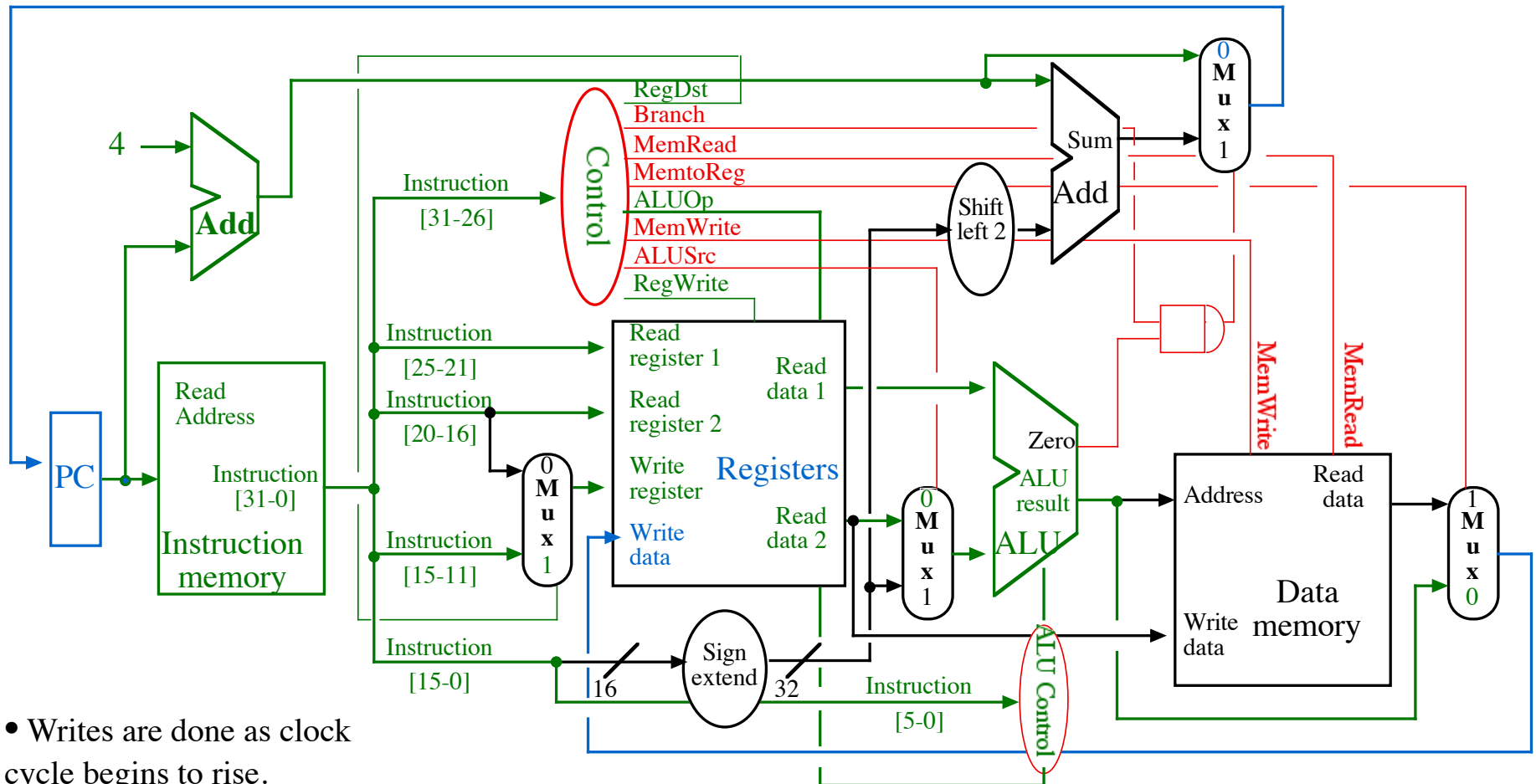
### Single-cycle Implementation (continued):

- R-Format instruction: Compute the answer.
  - Branch is 0; PC+4 written to PC.
  - ALU Result is written to Registers.




- Writes are done as clock cycle begins to rise.

I	op	rs	rt	16 bit number		
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-cycle Implementation (continued):

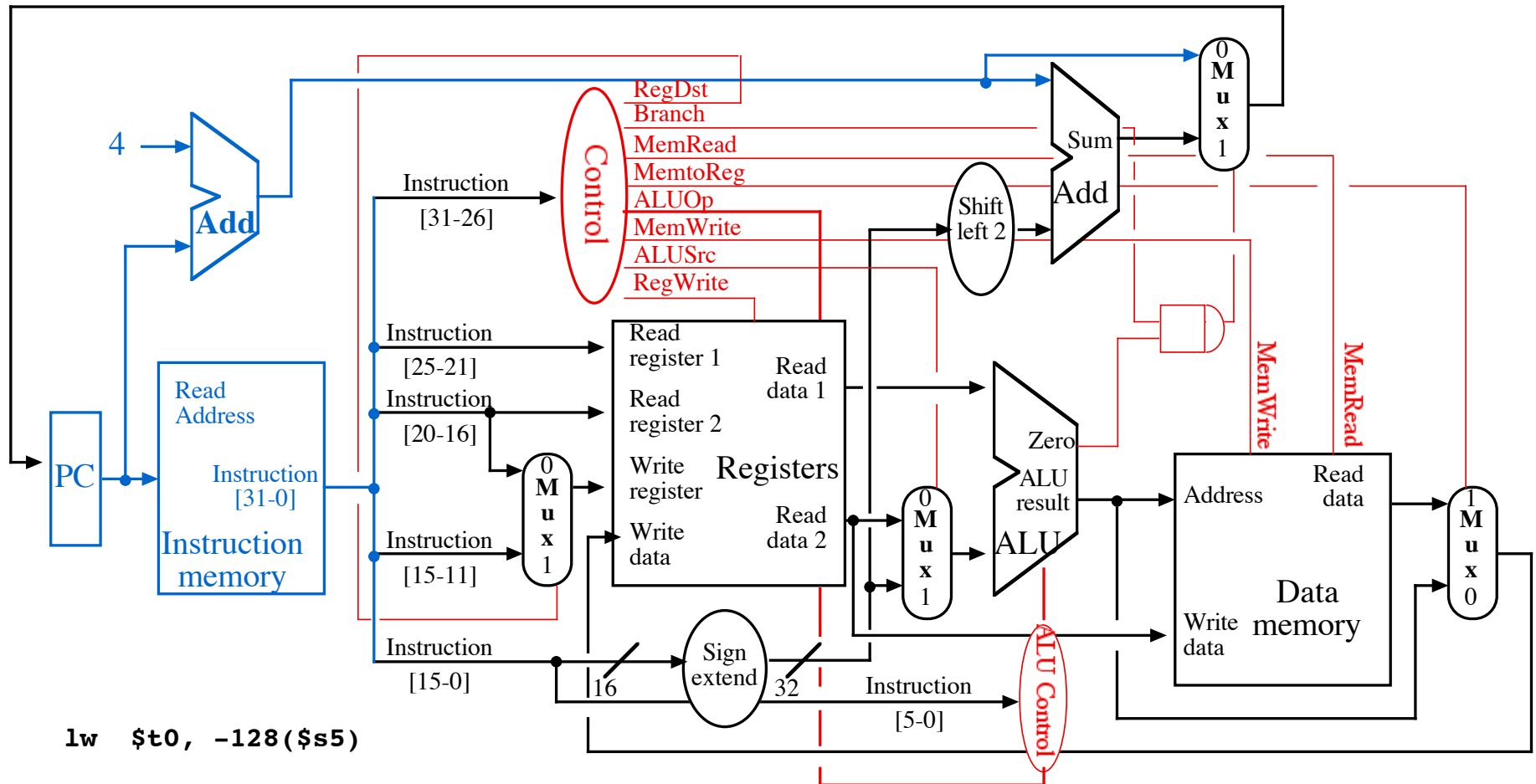- I-Format instruction: **lw**, **sw**.
- Fetch: Get instruction from memory and increment PC.
- Fetch is exactly the same as for R-Format.
- This is the same figure as Slide 11.






I	op	rs	rt	16 bit number		
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-cycle Implementation (continued):

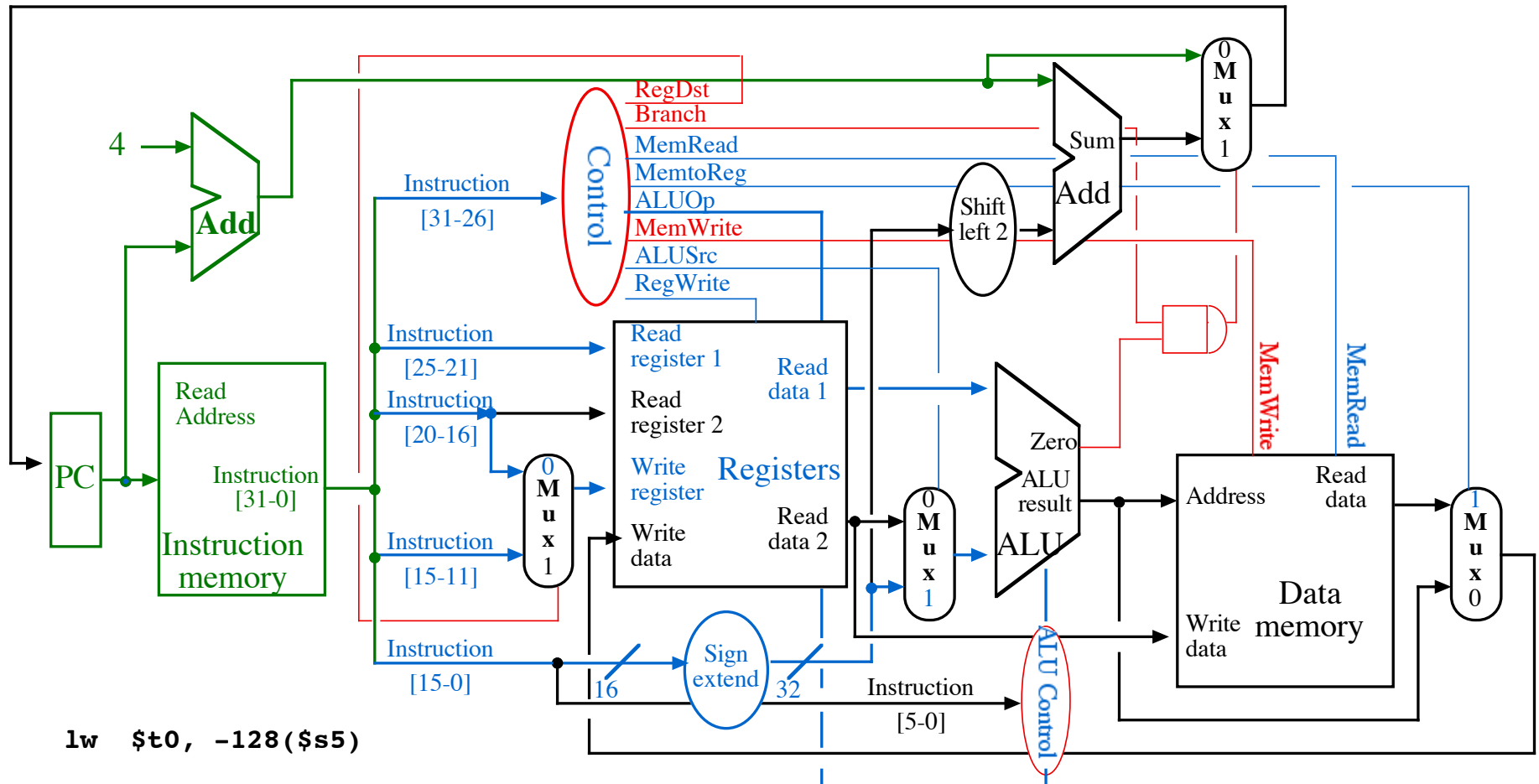- I-Format instruction: Load word.
- One register is read and sent to ALU.
- Second register specifies the register to write result.
- Offset is sign-extended and sent to ALU.




I	op	rs	rt	16 bit number		
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-cycle Implementation (continued):

- I-Format instruction: Load word.
- ALU completes operation.

**sw \$t3, 64(\$s7)**


**lw \$t0, -128(\$s5)**

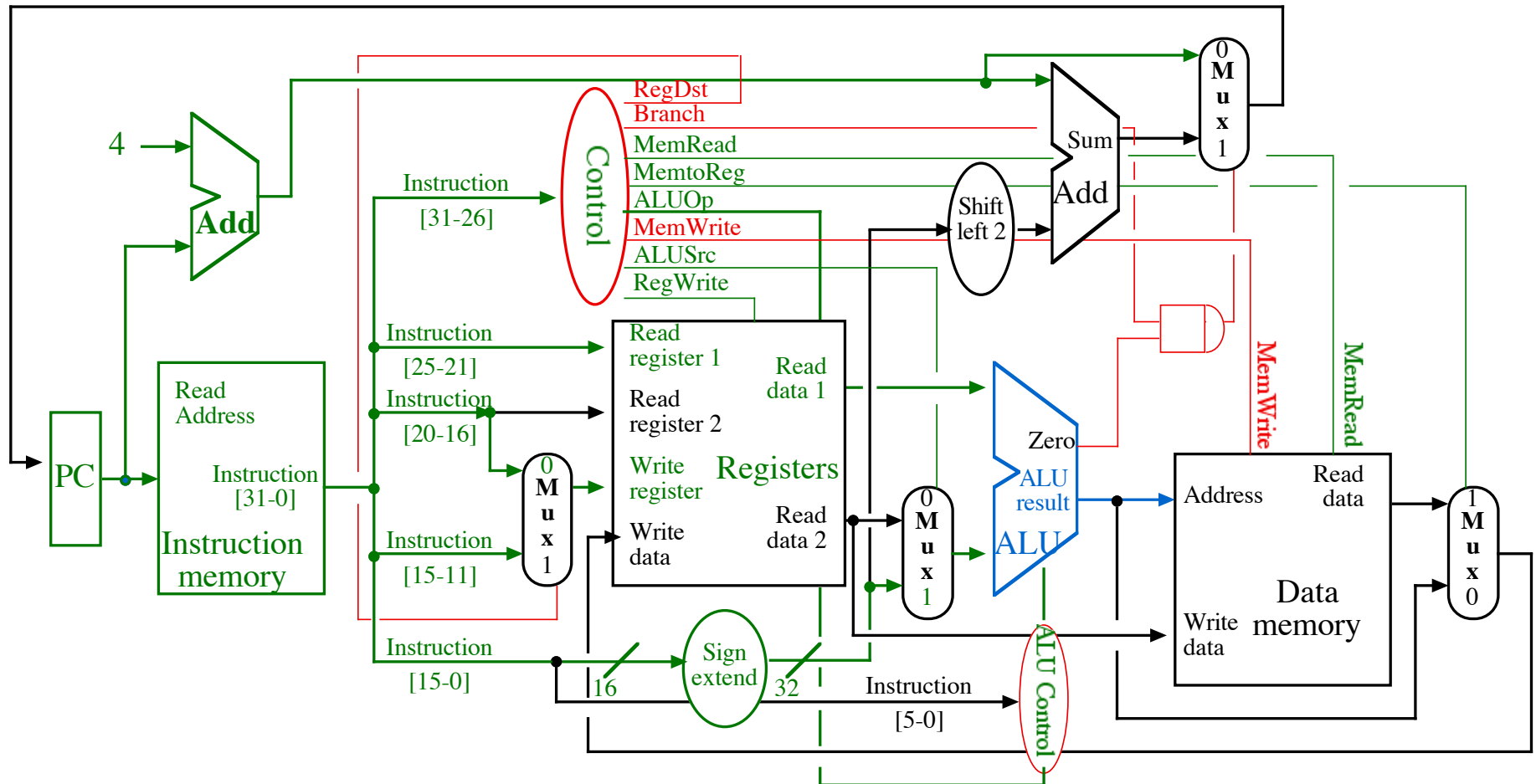

I	op	rs	rt	16 bit number		
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-cycle Implementation (continued):

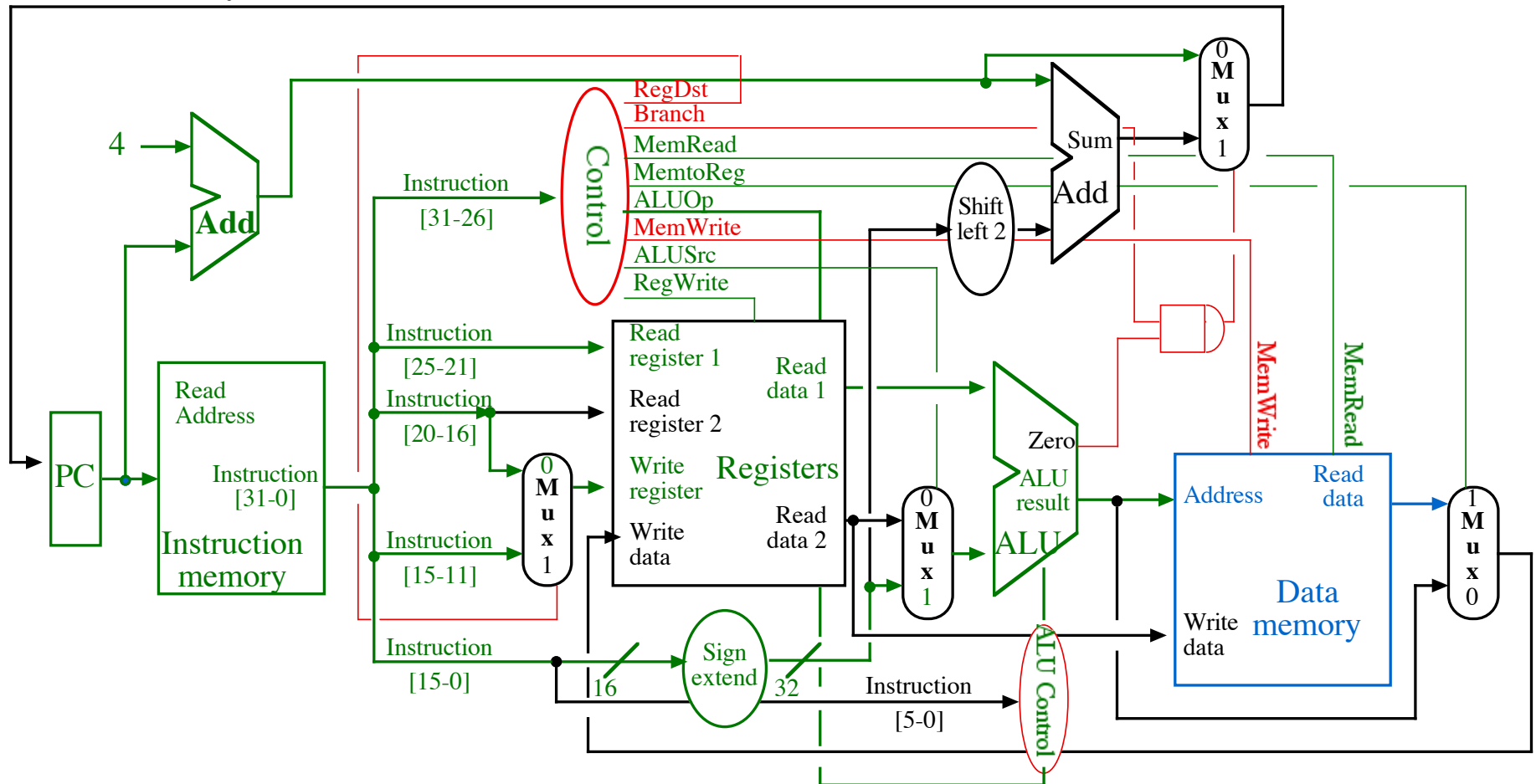- I-Format instruction: Load word.
- Data memory reads contents of Address.
- Data sent to Mux.






I	op	rs	rt	16 bit number		
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-cycle Implementation (continued):

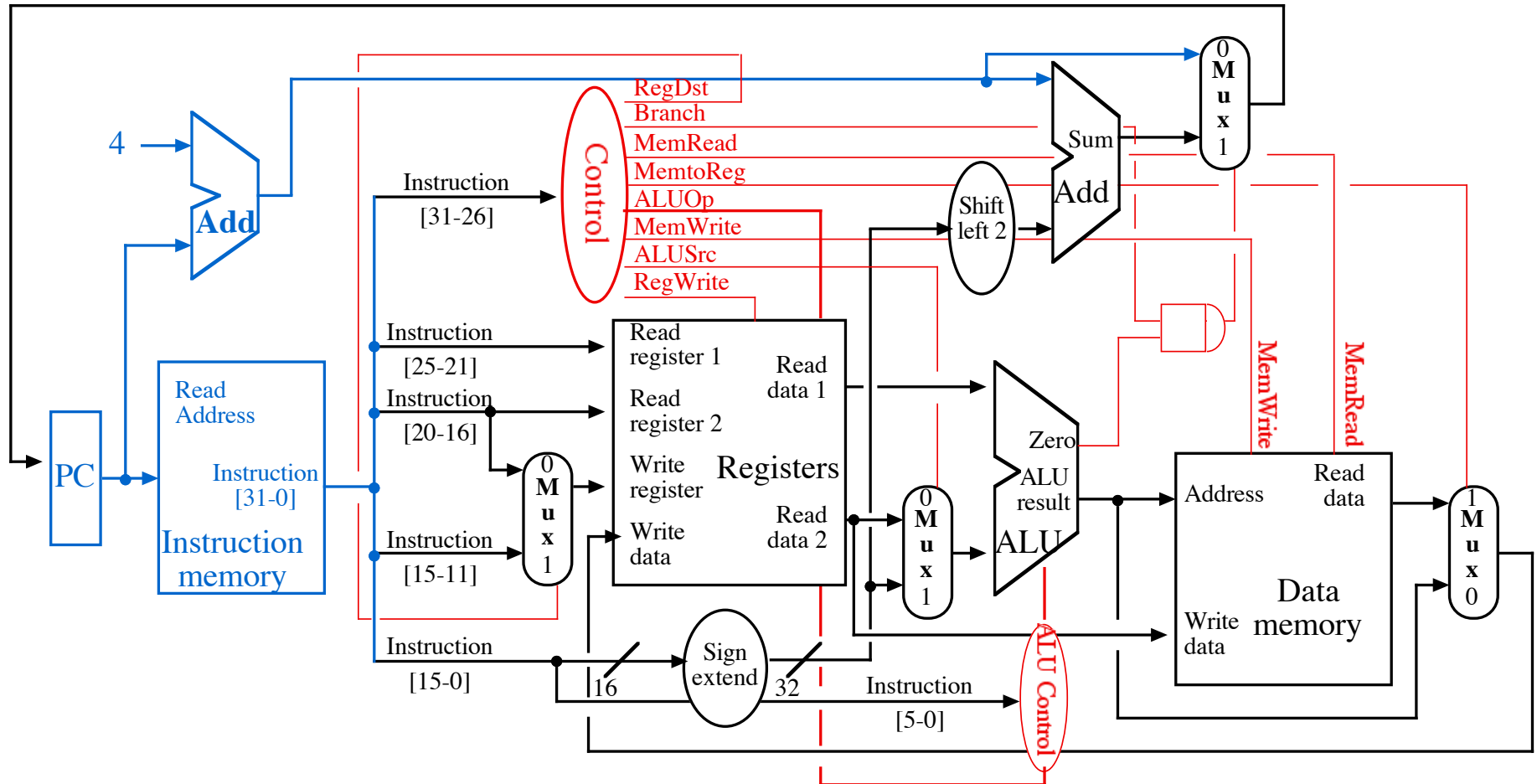- I-Format instruction: **beq**, Branch-if-Equal.
- Fetch: Get instruction from memory and increment PC.
- Fetch is exactly the same as for R-Format.
- This is the same figure as Slide 11.








I	op	rs	rt	16 bit number		
	6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Single-cycle Implementation (continued):

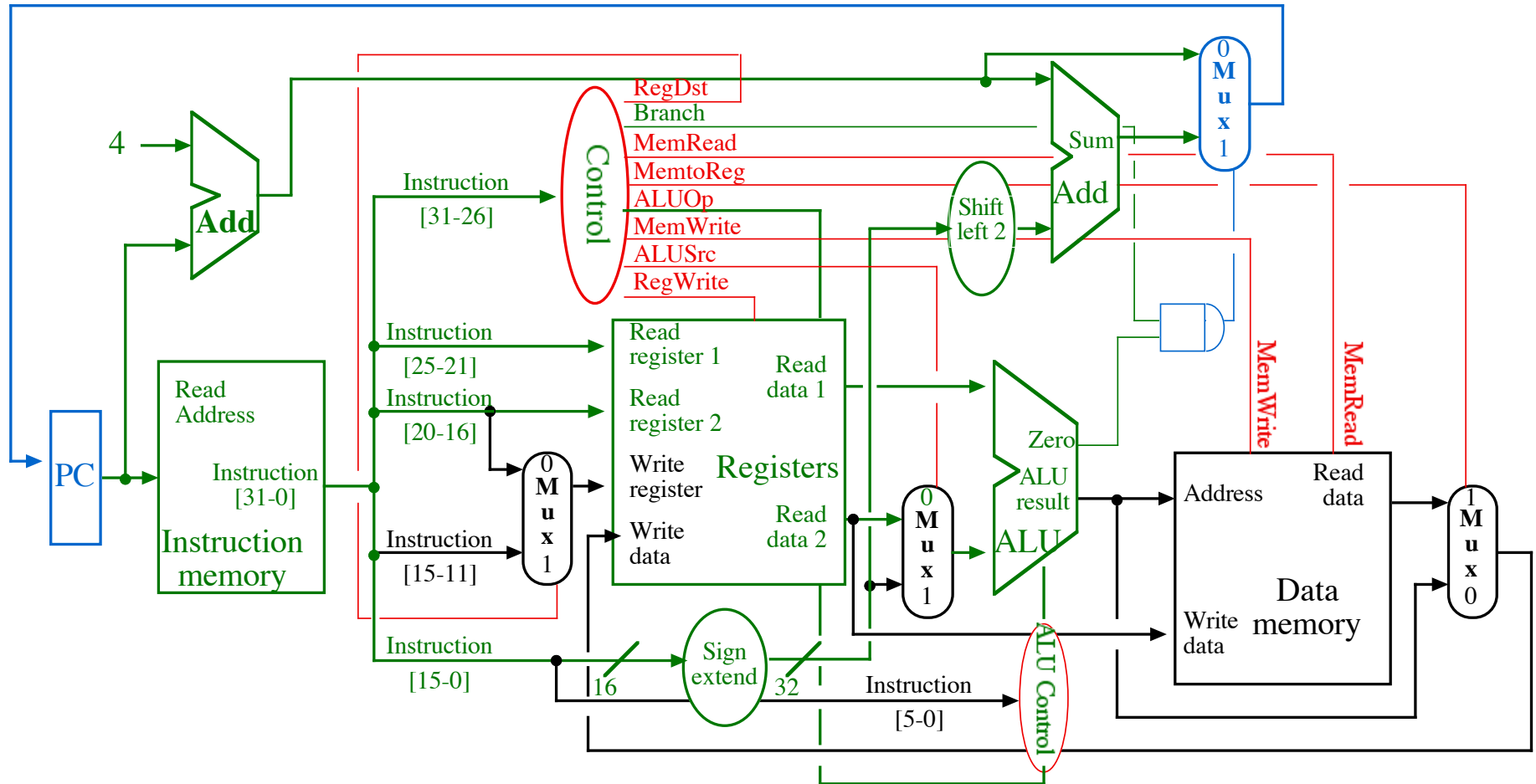
- I-Format instruction: **beq**, Branch-if-Equal.
- AND Gate determines result of Branch AND Zero.
- Mux triggered to send correct result to PC.
- PC not updated until rising edge of clock cycle.





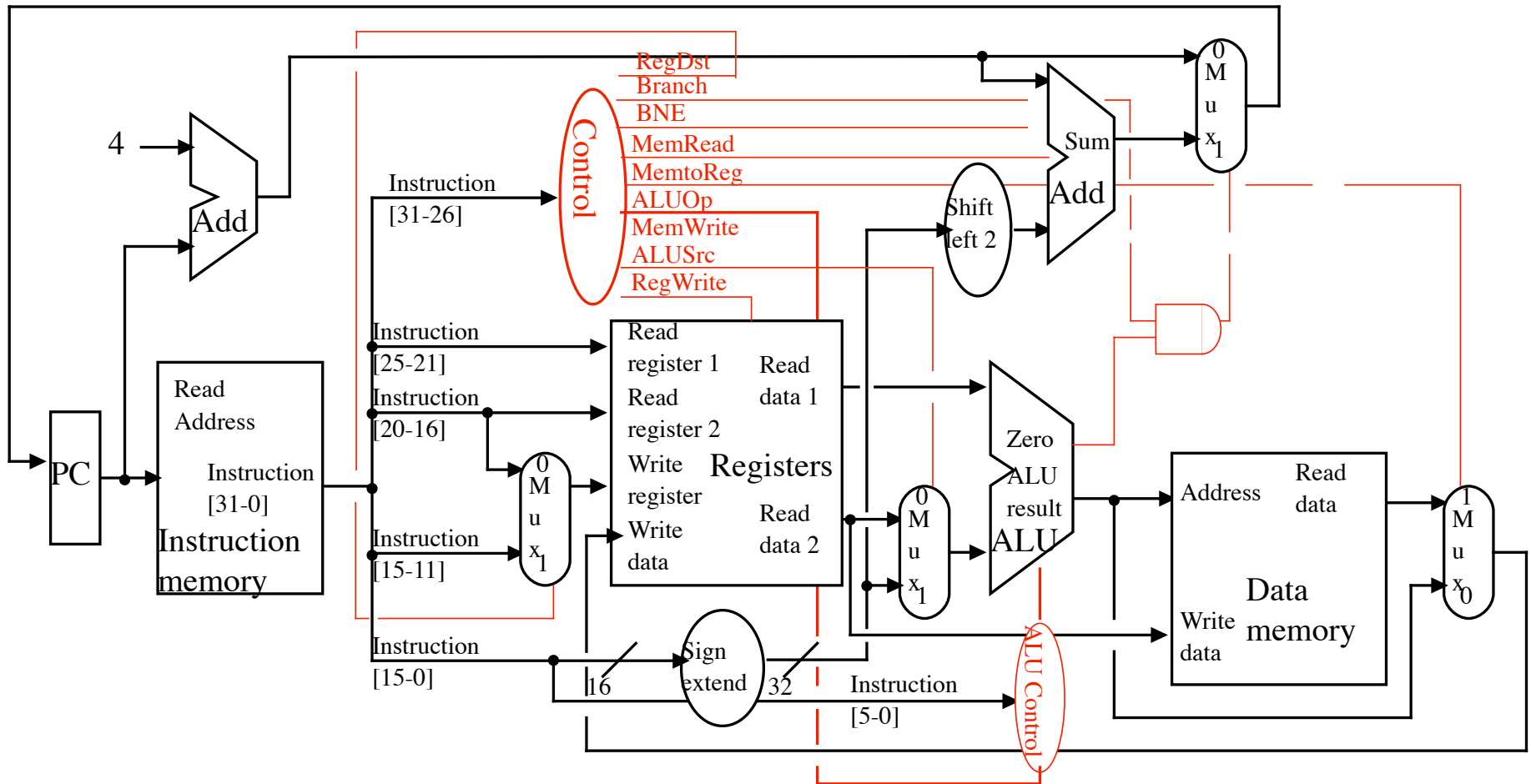
### Single-cycle Implementation (continued):

- I-Format instruction: **bne**, Branch-if-Not-Equal.
- What is changed/added?



 


Single-cycle Implementation (continued):

- J-Format instruction: **j**, jump.

- Extra items: Shift left 2, Mux.

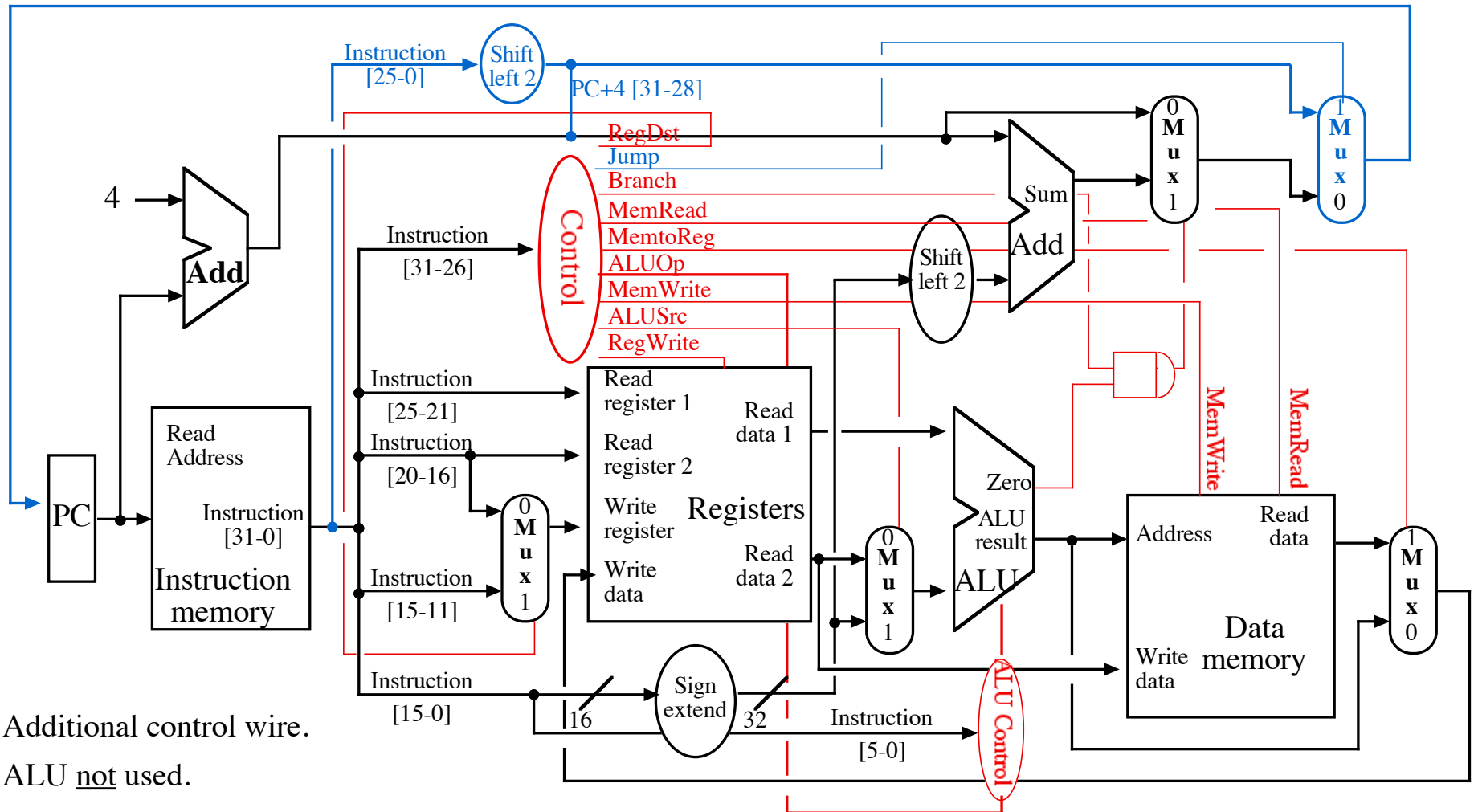- 26 bits shifted to give 28 bits + 4 bits from PC+4.



- Additional control wire.
- ALU not used.